

Logic Testing: Test Generation

Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: viren@ee.iitb.ac.in

CS-226: Digital Logic Design




Lecture 32-C: 20 April 2021

CADSL

Test Generation

Objective

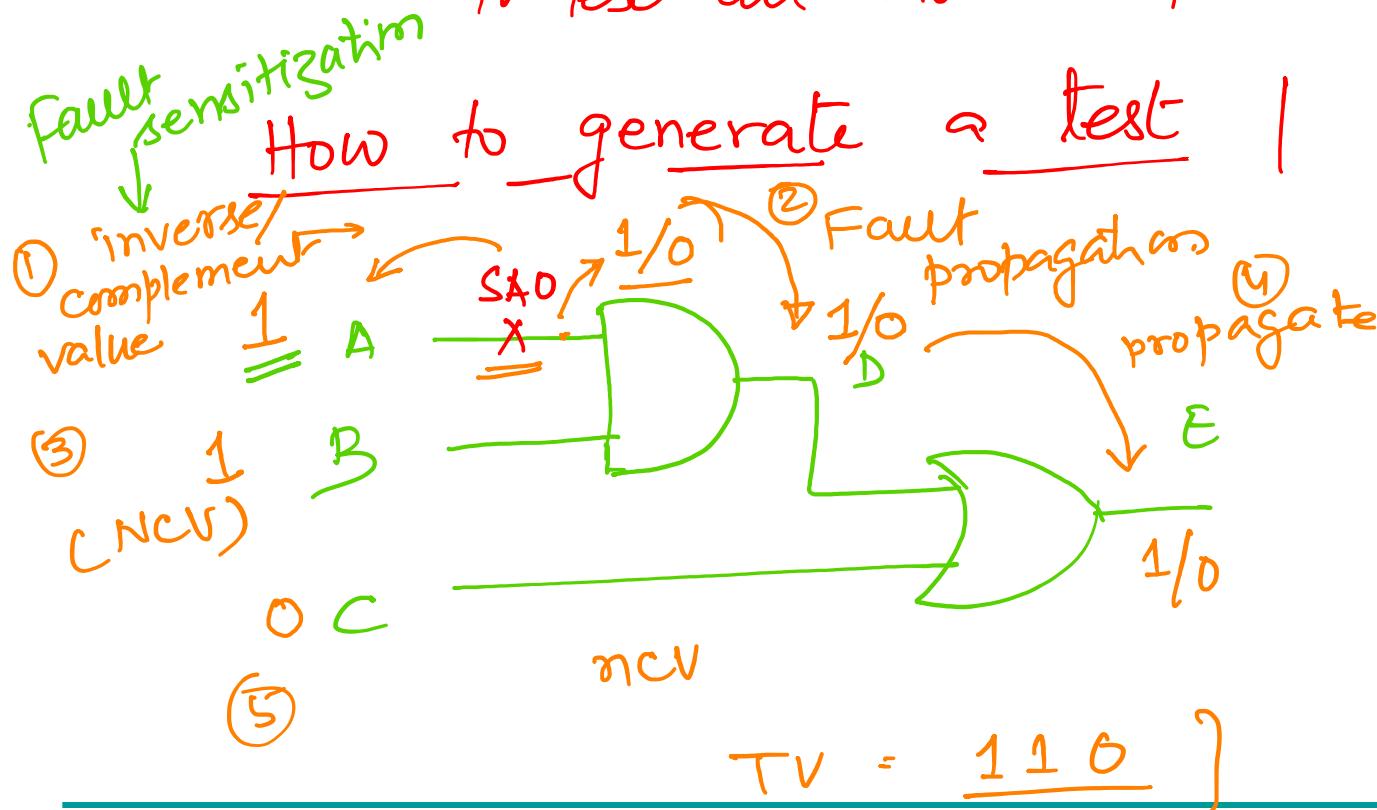Find the minimum no. of test vectors
to test all modeled faults of a circuit




Test Generation

- ① Define the fault location (net & type of fault)
- ② Activate/Sensitize the fault (having complementary value. jhor before fault site)
- ③ Propagate the fault effect towards PO (primary output)
- ④ need new assignment at the gates which are in propagation paths
- ⑤ If fault effect reaches to PO, - done
Input Assignment is Test Vector (TV)



Test Generation

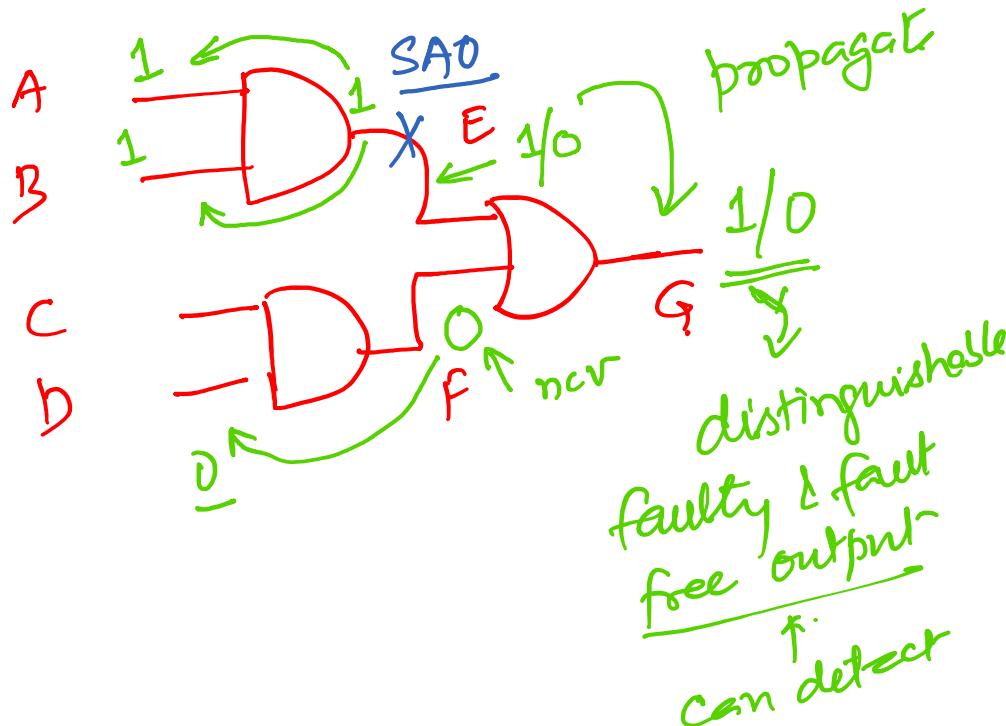

$A = 1 \quad B = 1$
Sensitize the fault

Propagation
nw at F
 $F = 0$

$$\text{IV} = \underline{\underline{1 \ 1 \ X \ 0}} \quad \left[\begin{array}{c} 1110 \\ 1100 \end{array} \right]$$

- ① ALGORITHMIC ✓
- ② ALGEBRAIC ✓



⇒ Boolean Difference

$$F(x_1, x_2 \dots x_i \dots x_n) = \underbrace{x_i f_{xi} \oplus \bar{x}_i f_{\bar{xi}}}$$

- Shannon's Expansion Theorem:

$$F(X_1, X_2, \dots, X_n) = X_2 \quad F(X_1, 1, \dots, X_n) + X_2 \quad F(\overline{X_1}, 0, \dots, X_n)$$

- Boolean Difference (partial derivative):

$$\frac{\partial F_j}{\partial g} = F_j(1, x_1, x_2, \dots, x_n) \oplus F_j(0, x_1, \dots, x_n)$$

Boolean Difference.

$$\frac{\partial f}{\partial x_i} = \underbrace{f_{xi} \oplus f_{\bar{xi}}}$$

- Fault Detection Requirements:


$$G(X_1, X_2, \dots, X_n) = 1$$

$$\frac{\partial F_j}{\partial g} = F_j(1, x_1, x_2, \dots, x_n) \oplus F_j(0, x_1, \dots, x_n) = 1$$



Test Generation

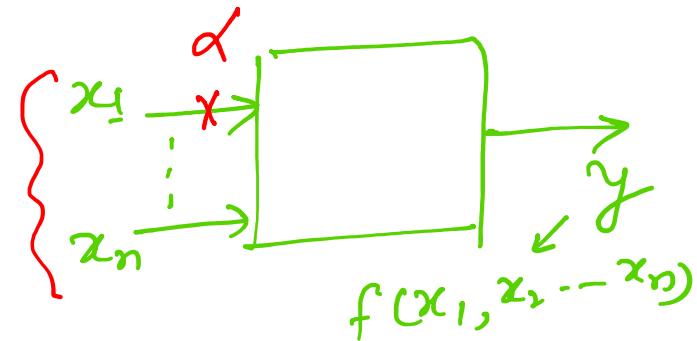An input assignment can be a test vector if it produces distinguishable faulty & fault free response.



$$y = f(x_1, x_2, \dots, x_i, \dots, x_n)$$

$$\boxed{f = \underline{x_i} f_{xi} + \overline{x_i} f_{\bar{x}_i}} \quad (\text{Shannon's expansion})$$

Assume there is a fault δ at $\underline{x_i}$

faulty output f_δ

$$\begin{aligned} \text{Fault - } \underline{x_i} \xrightarrow{\text{SAO}} f_\delta &= \underline{f_{\bar{x}_i}} \checkmark \\ \underline{x_i} \xrightarrow{\text{SAI}} f_\delta &= f_{xi} \checkmark \end{aligned}$$



Test Generation

$$f(x) \oplus f_{\bar{x}}(x) = 1$$

distinguishable

$f(x)$ $f_{\bar{x}}(x)$

$x = \underline{x_1, x_2, x_3, \dots, x_n}$

if x is a Test Vector

$$\underset{x_i}{x_i} f(x) \oplus \underset{\bar{x}_i}{\bar{x}_i} f_{\bar{x}_i}(x) \oplus \underset{=}{f_{\bar{x}}(x)} = 1$$

Let $x_i \leq 0$, $f_{\bar{x}}(x) = f_{\bar{x}_i}(x)$

$$\underset{x_i}{x_i} f_{x_i} \oplus \underset{\bar{x}_i}{\bar{x}_i} f_{\bar{x}_i} \oplus f_{\bar{x}_i} = 1$$

$$\underset{x_i}{x_i} f_{x_i} \oplus \underset{\bar{x}_i}{\bar{x}_i} f_{\bar{x}_i} \oplus (x_i \oplus \bar{x}_i) \cdot f_{\bar{x}_i} = 1$$

$(A \oplus A = 0)$

$$\underset{x_i}{x_i} f_{x_i} \oplus \underset{\bar{x}_i}{\bar{x}_i} f_{\bar{x}_i} \oplus \underset{\cancel{x_i}}{x_i} f_{\bar{x}_i} \oplus \underset{\cancel{\bar{x}_i}}{\bar{x}_i} f_{\bar{x}_i} = 1$$



Test Generation

$$x_i f_{ni} \oplus x_i f_{\bar{n}} = 1$$

$$x_i (f_{ni} \oplus f_{\bar{n}}) = 1$$

$$\boxed{x_i \cdot \frac{\partial f}{\partial x_i} = 1}$$

$$\checkmark x_i = 1 \leftarrow$$

Fault sensitization

$$\boxed{x_i = 0}$$

$$\frac{\partial f}{\partial x_i} = \boxed{f_{ni} \oplus f_{\bar{n}}} = 1$$

Fault propagation condition



Test Generation

$$x_i \leq 1 \quad f_x = f_{xi}$$

$$f(x) \oplus f_x(x) = 1$$

$$f(x) \oplus f_{\bar{x}_i}(x) = 1$$

$$x_i \cdot f_{xi} \oplus \bar{x}_i \cdot f_{\bar{x}_i} \oplus f_{\bar{x}_i} = 1$$

$$x_i \cdot f_{xi} \oplus \bar{x}_i \cdot f_{\bar{x}_i} \oplus (x_i \oplus \bar{x}_i) \cdot f_{\bar{x}_i} = 1$$

$$\cancel{x_i \cdot f_{xi}} \oplus \bar{x}_i \cdot f_{\bar{x}_i} \oplus \cancel{x_i \cdot f_{xi}} \oplus \bar{x}_i \cdot f_{\bar{x}_i} = 1 \quad \checkmark$$

$$\bar{x}_i \cdot f_{\bar{x}_i} \oplus \bar{x}_i \cdot f_{xi} = 1 \Rightarrow \bar{x}_i (f_{xi} \oplus f_{\bar{x}_i}) = 1$$

$$\bar{x}_i = 1 \Rightarrow x_i = 0 \rightarrow \text{Fault sensitization}$$

$$? \quad \frac{\partial f}{\partial x_i} = f_{xi} \oplus f_{\bar{x}_i} = 1 \rightarrow \text{Fault propagation.}$$

$$x = x_1 \cdot x_2 \cdot x_i \cdots x_n \rightarrow \checkmark$$



Boolean Difference

$$f(x_1, \dots, x_i = 0, \dots, x_n) \oplus f(x_1, \dots, x_i = 1, \dots, x_n) = 1$$

- Represented by the symbol $\underline{df(x)/dx}$
- $df(x)/dx_i$ for $x=0$ and $df(x)/dx_i$ for $x=1$ are called *the residues/co-factors* of the function for $x = x_i$
- One of the residue is the good-circuit value and the other is the faulty-circuit value for x_i
- To detect the fault, the two residues should be complementary
- Solving the equation yield the values of the primary inputs to detect a stuck-at fault on x_i
- The test pattern is: $x_i df(x)/dx_i = 1$ & $x_i' df(x)/dx_i = 1$

Fault propagation



Test Generation



$$e = f(a, b, c) = \underline{\overline{ab} + c}$$

$$\stackrel{TV}{=} a \cdot \frac{\partial f}{\partial a} = 1$$

$$a=1 \text{ and } \underline{f_a \oplus f_{\bar{a}} = 1}$$

$$f_a = b + c$$

$$f_{\bar{a}} = c$$

$$a \cdot ((b+c) \oplus c) = 1$$

$$a \cdot ((b+c)\bar{c} + (\overline{b+c}) \cdot c) = 1$$

$$\Rightarrow a \cdot (b\bar{c} + 0 + \cancel{b \cdot \bar{c} \cdot c}) = 1 \Rightarrow \boxed{a \cdot b \cdot \bar{c} = 1}$$


$$\left. \begin{array}{l} a=1 \\ b=1 \\ \bar{c}=1 \end{array} \right\} \left. \begin{array}{l} a=1 \\ b=1 \\ c=0 \end{array} \right\} \stackrel{TV}{=}$$



Test Generation

$$f(x) = f(x_1, x_2, \dots, x_i, \dots, x_n, h) \rightarrow$$

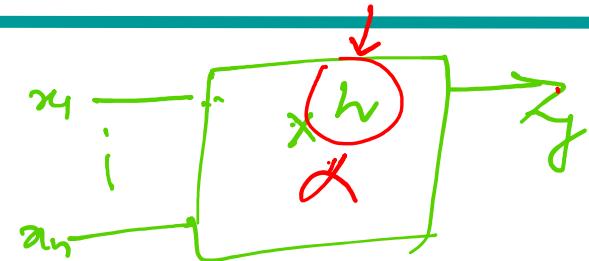$f_d \rightarrow$ faulted ~~or~~ function
(fault at h)



$$\underline{h} = f(\underline{x}, \underline{x} \dots, \underline{x_n})$$

$$\underline{f(x,h)} \oplus \underline{f_d(x,h)} = 1$$

$$\text{for cert } h \text{ is } \underline{\text{so}} \quad f_d(x,h) = \underline{f_h(x,h)}$$

$$\underline{f(x,h)} \oplus \underline{f_h(x,h)} = 1$$

$$h f_h \oplus \bar{h} f_{\bar{h}} \oplus f_{\bar{h}} = 1$$

$$h f_h \oplus \bar{h} f_{\bar{h}} \oplus (h \oplus \bar{h}) f_{\bar{h}} = 1$$

$$h f_h \oplus \cancel{\bar{h} f_{\bar{h}}} \oplus \cancel{h f_{\bar{h}}} \oplus \cancel{\bar{h} f_h} = 1 \Rightarrow h(f_h \oplus f_{\bar{h}}) = 1$$

$$h=1 \checkmark$$

$$\frac{\partial f}{\partial h} = 1 \checkmark$$

↑



Test Generation

$\lambda \text{ sao}$


$$\lambda \cdot (f_h \oplus f_{\bar{h}}) = 1$$

if $\lambda \text{ is sat}$ $f_x = f_h$

then


$$\bar{\lambda} (f_h \oplus f_{\bar{h}}) = \bar{\lambda} \frac{\partial f}{\partial h} = 1$$
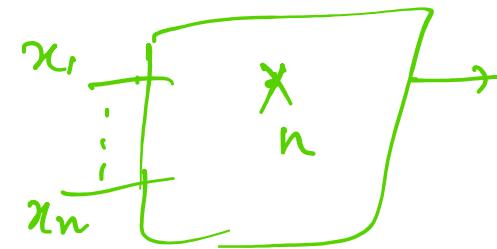
$$\boxed{\begin{aligned}\bar{\lambda} &= 1 \\ \frac{\partial f}{\partial h} &= 1\end{aligned}}$$



Fault Detection

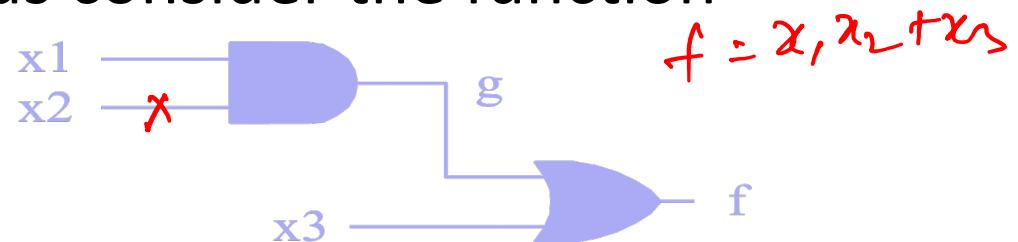
- ❖ $x_i, df(x)/dx_i = 1$ for s-a-0 at x_i
- ❖ $x_i', df(x)/dx_i = 1$ for s-a-1 at x_i
- ❖ As an example, let us consider the function



- ❖ $f(x) = x_1 x_2 + x_3$ ✓
- ❖ Thus $\underline{df(x)/dx_2} = \underline{x_3} \oplus (\underline{x_1} + \underline{x_3}) = \underline{x_3}' \underline{x_1} = 1$. Then
- ❖ $x_1 = 1$ and $x_3 = 0$.
- ❖ For the SA1 and SA0 faults on x_2 , the patterns are then $x_1 x_2 x_3 = (\underline{1}00)$ and $(1\underline{1}0)$, respectively.

Fault Detection
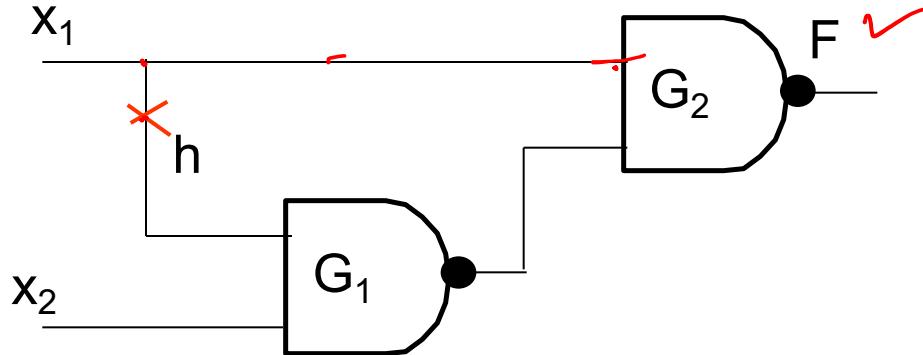
$$h(x) \cdot \frac{\partial f}{\partial h} = 1$$



S-a-0 fault at h

Test Vector

$$h(X) dF^*(X,h)/dh = 1$$

$$F(X,h) = x_1' + hx_2$$

$$h(X) = \underline{x_1'}$$


$$\begin{aligned} dF^*(X,h)/dh &= \underline{x_1'} \oplus (\underline{x_1'} + \underline{x_2}) \\ &= \underline{x_1x_2} \end{aligned}$$

$$\underline{x_1} \cdot \underline{x_1x_2} = \underline{x_1x_2} = 1$$



$$\begin{aligned} x_1 &= 1 \\ x_2 &= 1 \end{aligned} \quad \left. \begin{array}{l} T \\ V \end{array} \right.$$



Fault Detection

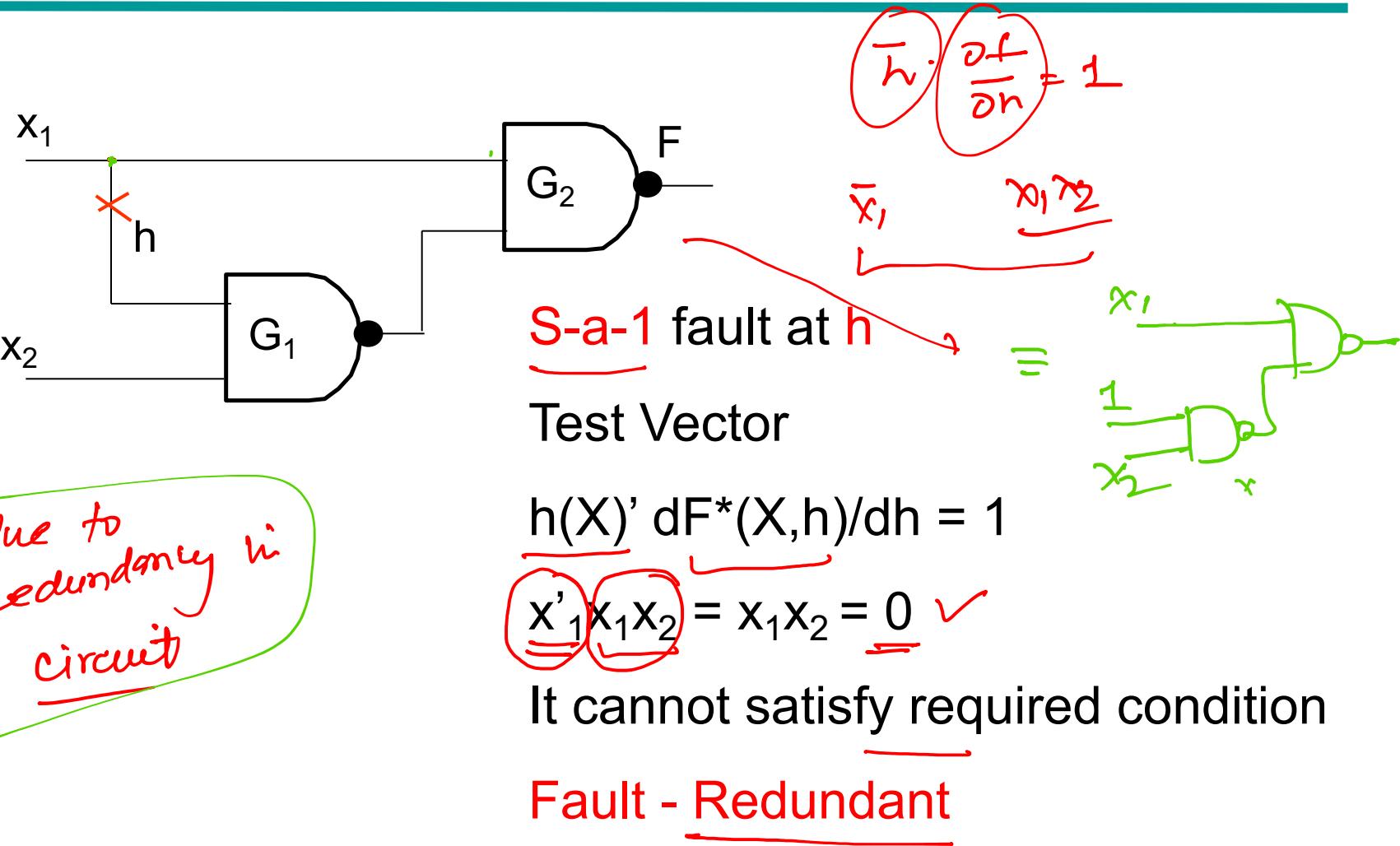

-Do

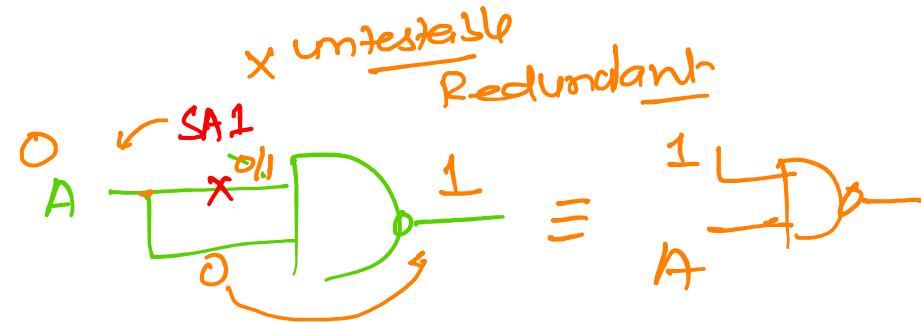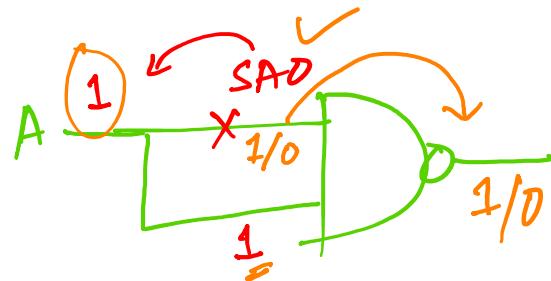

Redundant Faults

$$FC = \text{Fault Coverage} =$$

$$\frac{\# \text{ detectable faults}}{\# \text{ faults}}$$

$$FE = \text{Fault Efficiency} = \frac{\# \text{ detectable faults}}{\# \text{ faults} - \# \text{ Redundant faults}}$$

faults: 1000

990 - detectable

10 Redundant

✓

$$FC = \frac{990 \times 100}{1000}$$

$$= 99\%$$

$$FE = \frac{990}{1000-10} = 100\%$$



Boolean Difference \rightarrow TV or Redundant
— Test Efficiency = 100%
— Fault

Algorithmic method — Backtracking

Test vectors must be small!

TE/PE $\approx 100\%$

Reconvergent fanout.

Fanouts free
circuit.



Thank You

