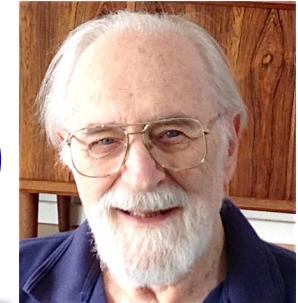


Logic Optimization: Karnaugh Map



Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: viren@ee.iitb.ac.in

CS-226: Digital Logic Design




Lecture 15-B: 18 February 2021

CADSL

Minimum Sum of Products (MSOP)

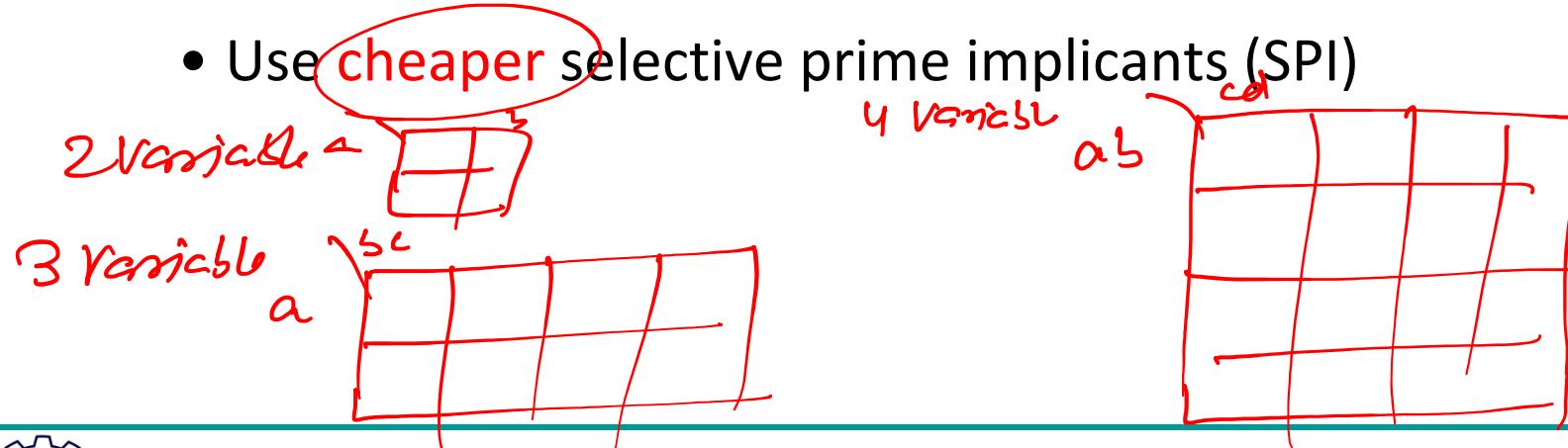- Identify all prime implicants (PI) by letting minterms and implicants grow.
- Construct MSOP with PI only :
 - Cover all minterms
 - Use only essential prime implicants (EPI)
 - Use **no** redundant prime implicant (RPI)
 - Use **cheaper** selective prime implicants (SPI)



Five-Variable Function

- $F(A, B, C, D, E)$

$$\frac{0-15}{A=0}$$

$$\frac{16-31}{A=1}$$



$$= \sum m(0, 1, 4, 5, 6, 13, 14, 15, 22, 24, 25, 28, 29, 30, 31)$$

$$A = 0$$

$$B$$

$$A = 1$$

$$B$$

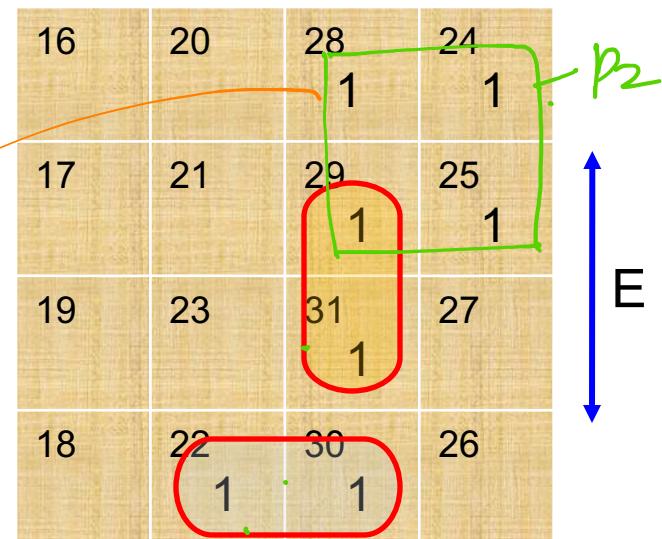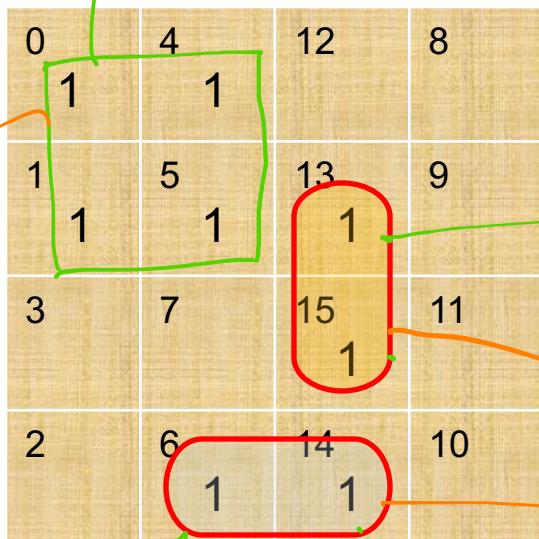


$$F = \overline{A} \overline{B} \overline{D} + A B \overline{D} + B C E + C D \overline{E}$$



Why Not More Than Five Variables?



- Too hard to visualize in 3+ dimensions
- Systematic approach:
"Tabular Methods"
 - Used in computer programs
- Why K-Maps at all?
 - Faster for quick optimizations
 - Understand Boolean logic and HW design
 - Design with simplification in mind

Six-Variable K-Map

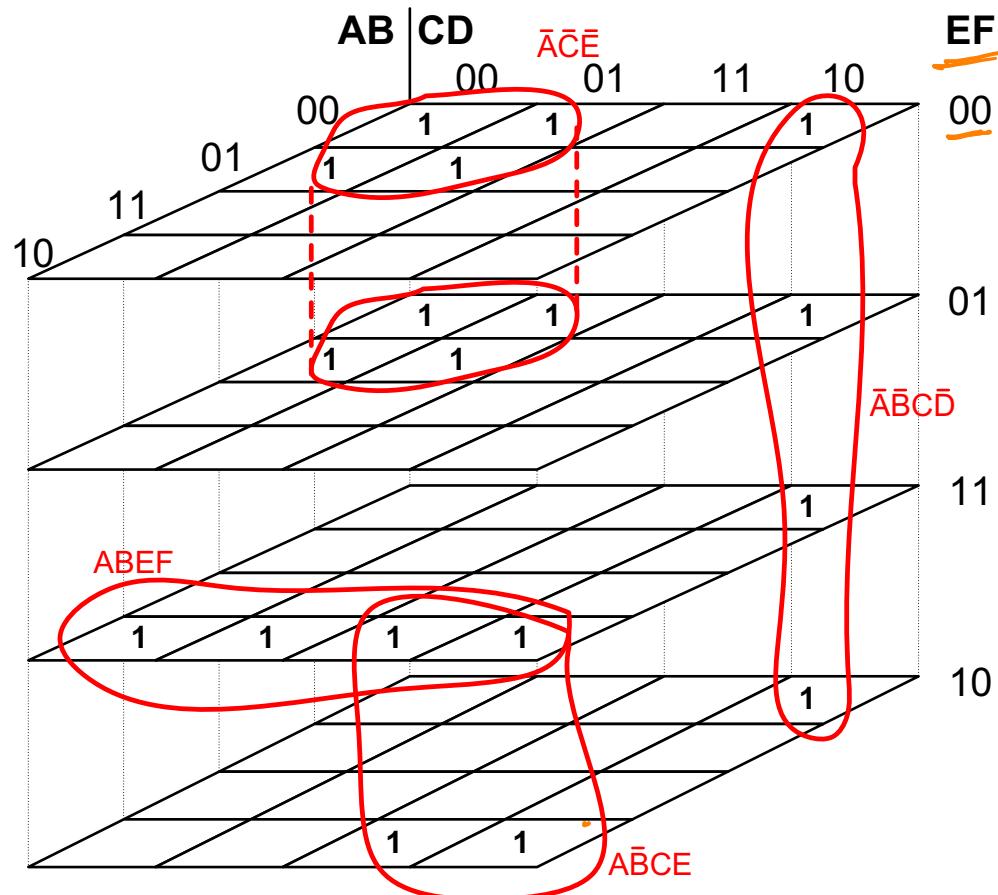


Functions with Don't Care Minterms

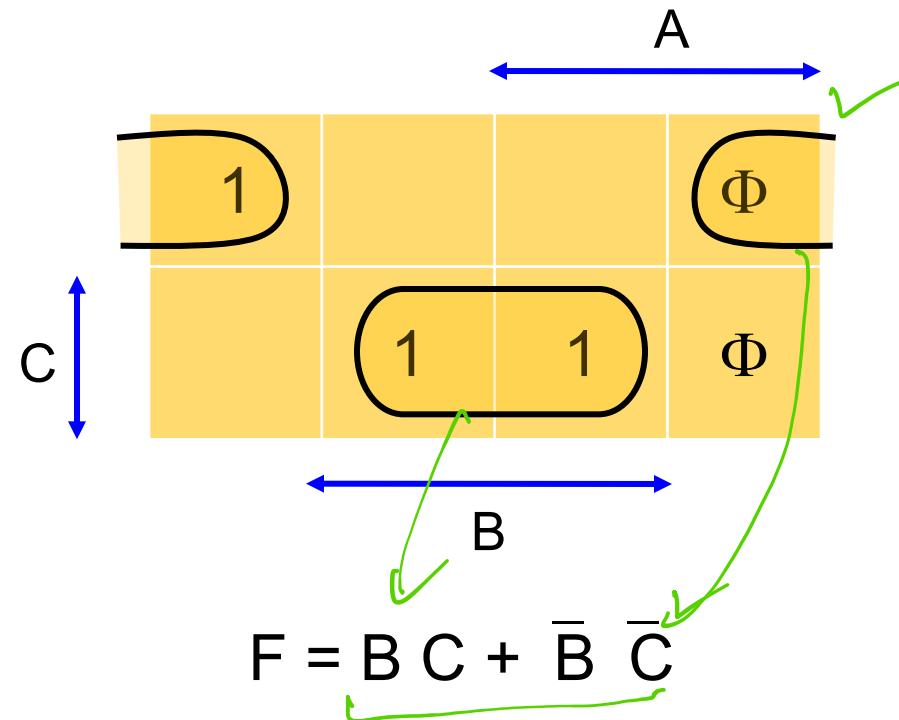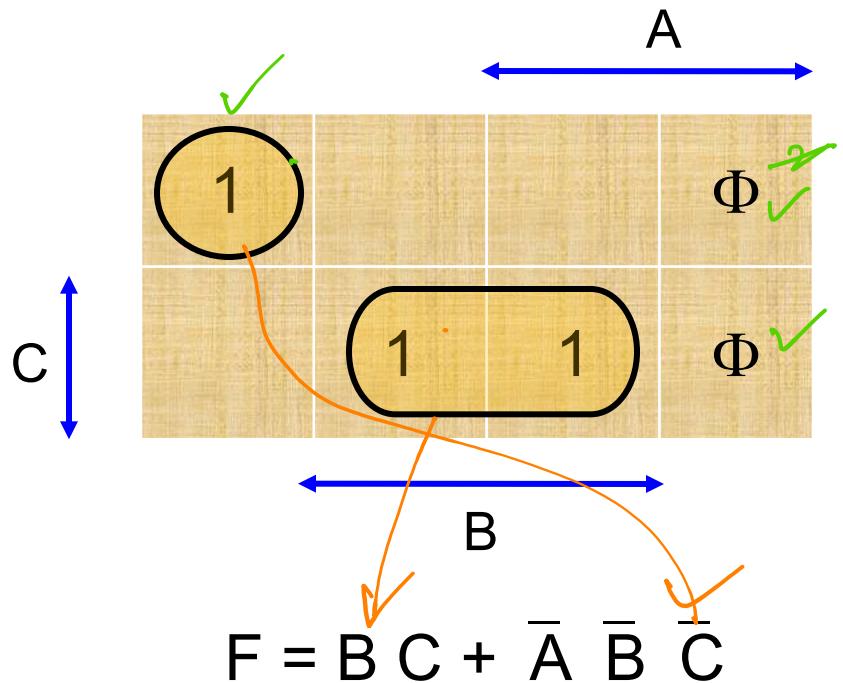- $F(A,B,C) = \sum m(0,3,7) + d(4,5)$
- Include don't care minterms when beneficial.




Minimized SOP and POS

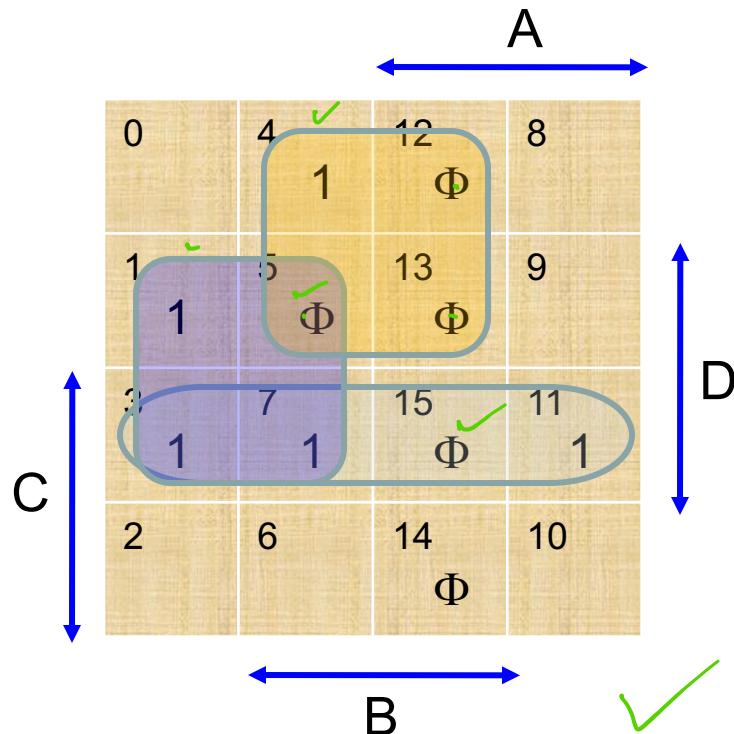- $$\begin{aligned} F(A,B,C,D) &= \sum m(1,3,4,7,11) + d(5,12,13,14,15) \\ &= \prod M(0,2,6,8,9,10) \ D(5,12,13,14,15) \end{aligned}$$



$$F = B \bar{C} + \bar{A}D + CD$$

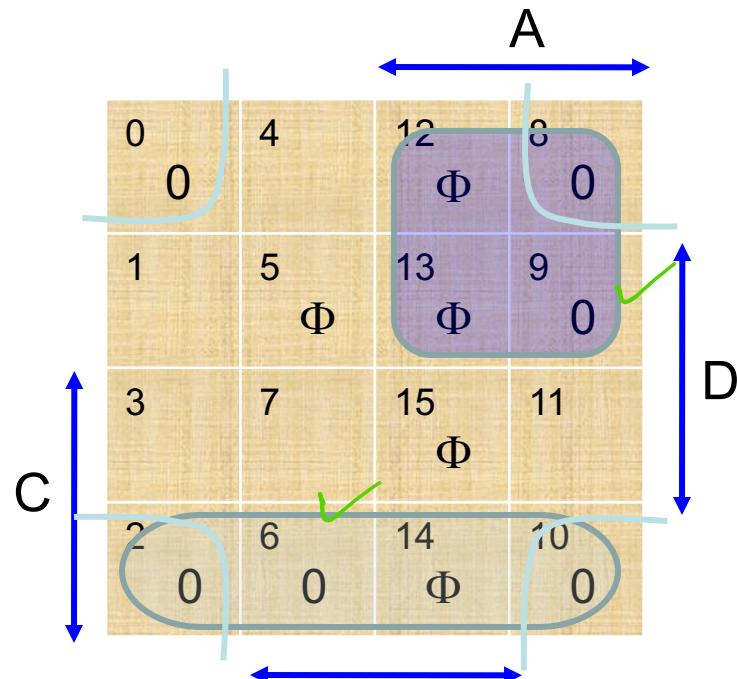

$$\begin{aligned} \bar{F} &= \bar{B} \bar{D} + C \bar{D} + A \bar{C} \\ F &= (B + D)(\bar{C} + D)(\bar{A} + C) \end{aligned}$$





SOP and POS Circuits

$$\bullet F(A,B,C,D) = \sum m(1,3,4,7,11) + d(5,12,13,14,15)$$

M_{SOP} *m_{in}*

$$= \prod M(0,2,6,8,9,10) D(5,12,13,14,15)$$

M_{POS}

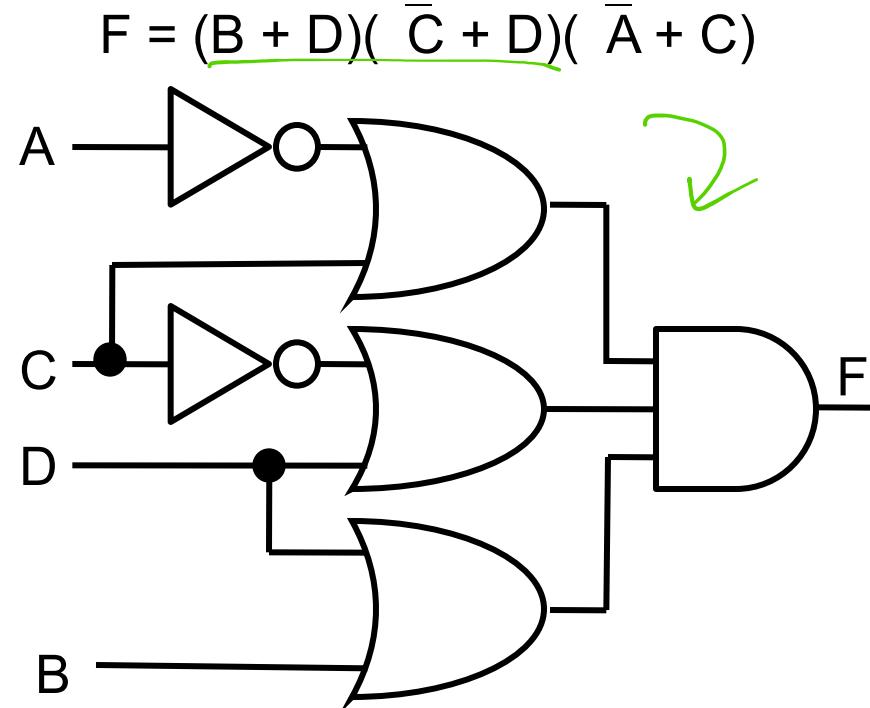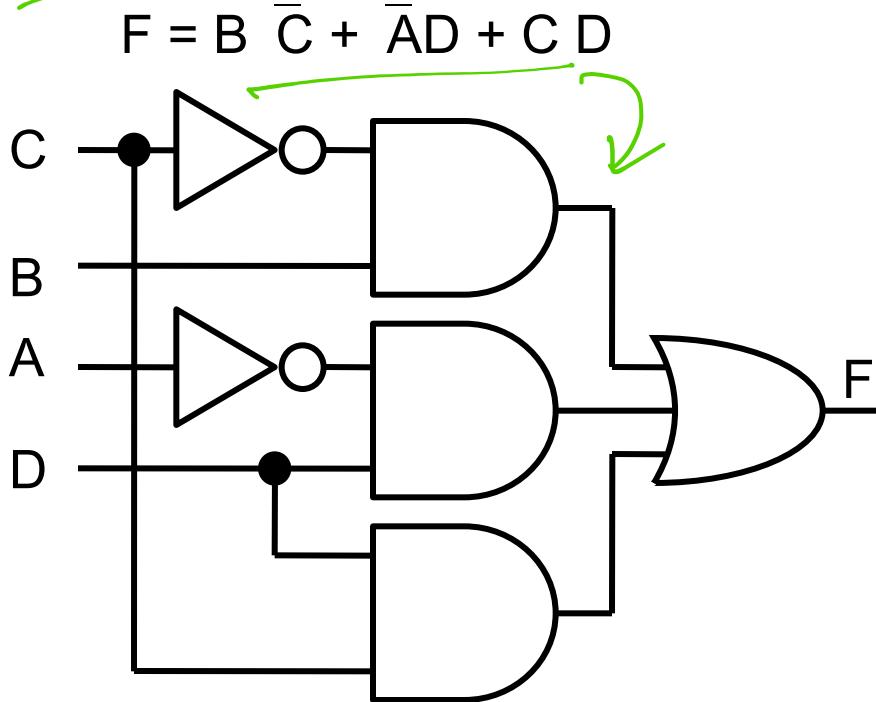

Multiple- Output Minimization



Multiple-Output Minimization

Inputs				Outputs	
A	B	C	D	F1	F2
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	1	1

$F_1(A, B, C, D)$

$F_2(A, B, C, D)$




Individual Output Minimization


Need five products.

11 literals

F1

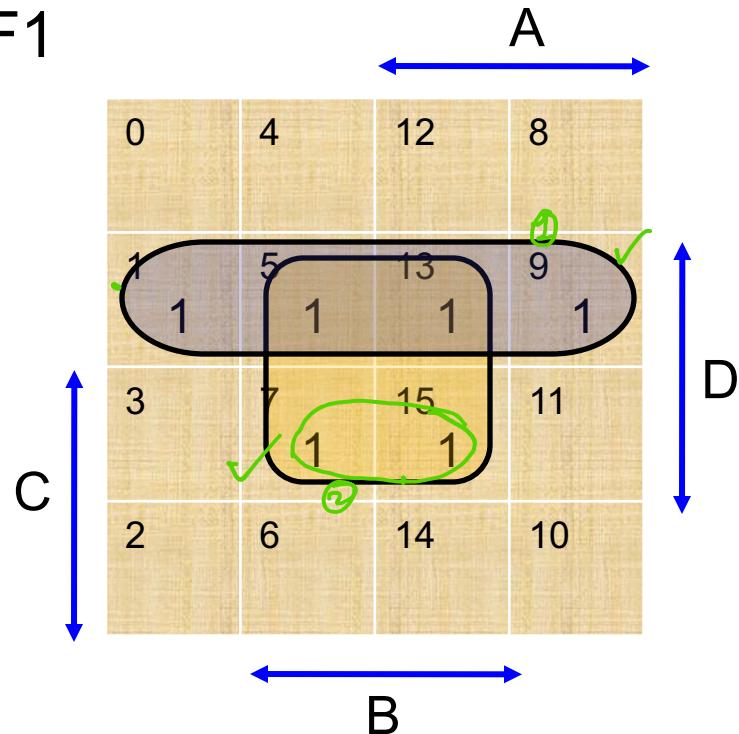

F2

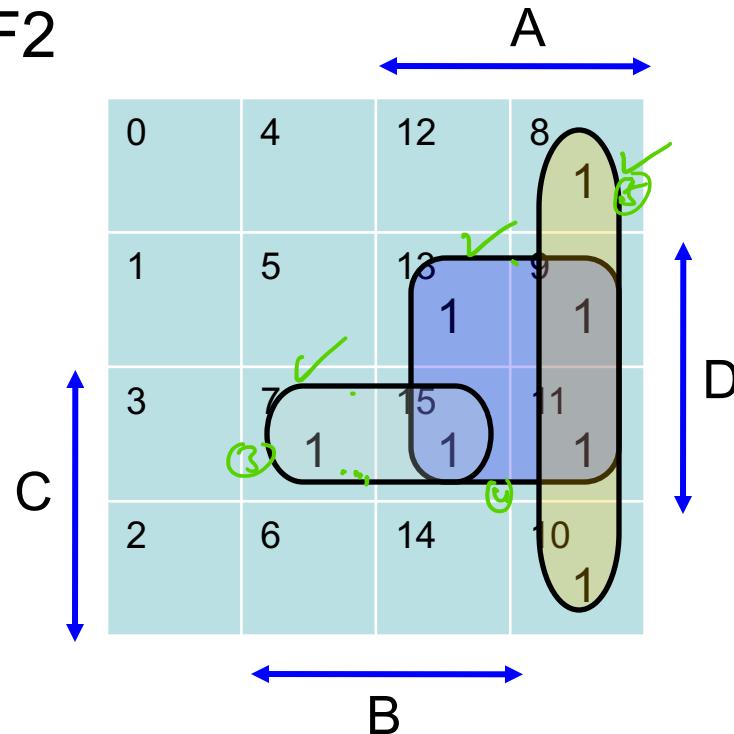

Global Minimization

Need four products.

~~11~~ 9 liters

F1

A

0	4	12	8
1	5	13	9
3	7	15	11
2	6	14	10

C

B

F2

A

0	4	12	8
1	5	13	1
3	7	15	1
2	6	14	10

D

C

B




Reed Muller

Representation



Reed Muller Representation

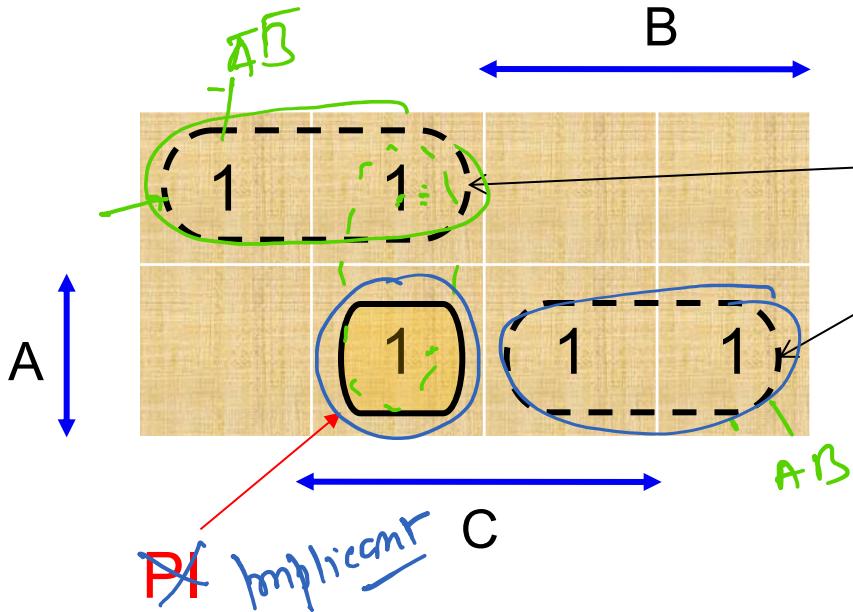

MSOP:

$$\overline{A}\overline{B} + A\overline{B} + \overline{B}C$$
$$= \overline{A}\overline{B} + A\overline{B} + A\overline{B}C$$

disjoint SOP
+ $\rightarrow \oplus$

$$F = \overline{A}\overline{B} \oplus A\overline{B} \oplus A\overline{B}C$$

$$F: (1 \oplus A)(B \oplus 1) \oplus A \cdot B \oplus A \cdot (B \oplus 1) \cdot C$$

$$F: 1 \oplus A \oplus B \oplus AC \oplus ABC$$



Reed Muller Representation

$$\begin{aligned} & (A \oplus 1)(B \oplus 1) \oplus AB \oplus AC(B \oplus 1) \\ &= 1 \oplus A \oplus B \oplus \cancel{AB} \oplus \cancel{ACB} \oplus AC \end{aligned}$$


$$F = 1 \oplus A \oplus B \oplus AC \oplus ABC$$

RM Representation



Reed Muller Representation
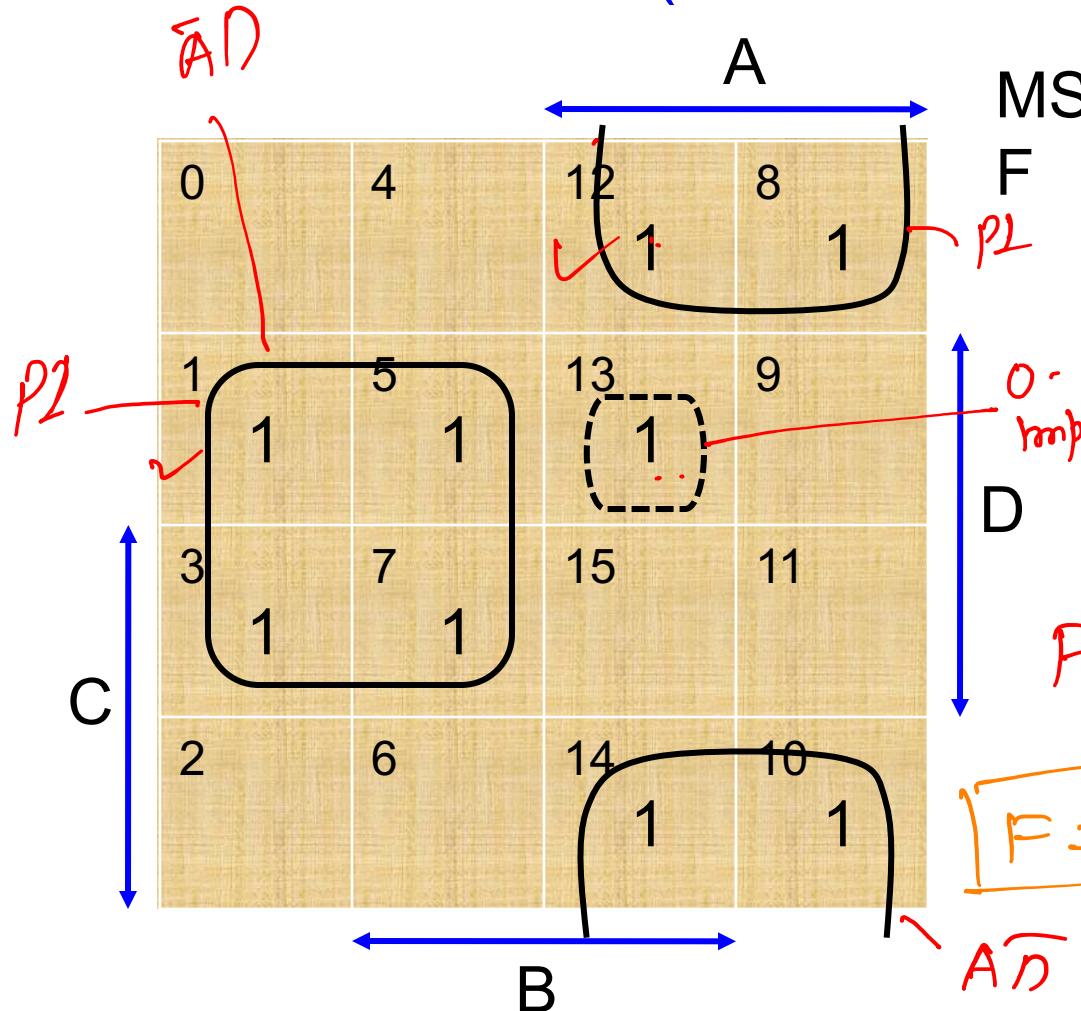
$$F = \sum m(1, 3, 5, 7, 8, 10, 12, 13, 14)$$



MSOP:

$$F = \bar{A}D + A\bar{D} + AB\bar{C}D$$

$O\text{-Implicant } AB\bar{C}D$

$$F = \bar{A}D \oplus A\bar{D} \oplus AB\bar{C}D$$

$$F = A \oplus D \oplus ABD \oplus ABCD$$

↑ R-M

Canonical,



Reed Muller Representation

$$\begin{aligned} F &= \overline{AD} \oplus \overline{A}\overline{D} \oplus A\overline{B}\overline{C}\overline{D} \\ &= (1 \oplus A) \cdot \overline{D} \oplus A \cdot (1 \oplus \overline{D}) \oplus A\overline{B}D(1 \oplus C) \\ &= D \oplus \cancel{A}\cancel{D} \oplus A \oplus \cancel{A}\cancel{D} \oplus A\overline{B}D \oplus A\overline{B}C\overline{D} \end{aligned}$$

$$F = A \oplus D \oplus A\overline{B}D \oplus A\overline{B}C\overline{D}$$

RM expression



Thank You

