

# Multiple-Level Optimization

---

Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: [viren@ee.iitb.ac.in](mailto:viren@ee.iitb.ac.in)

*EE-224: Digital Logic Design*

---



*Lecture 27-A: 07 March 2021*

**CADSL**

# Multiple-Level Optimization

---

- Multiple-level circuits are circuits that have more than two level (plus input and/or output inverters)
- For a given function, **multiple-level circuits can have reduced gate input cost compared to two-level (SOP and POS) circuits**
- Multiple-level optimization is performed by applying transformations to circuits represented by equations while evaluating cost



# Transformations

---

- **Factoring** - finding a factored form from SOP or POS expression
  - Algebraic - No use of axioms specific to Boolean algebra such as complements or idempotence
  - Boolean - Uses axioms unique to Boolean algebra
- **Decomposition** - expression of a function as a set of new functions



# Transformations (continued)

---

- Substitution of G into F - expression function F as a function of G and some or all of its original variables
- **Extraction** - decomposition applied to multiple functions simultaneously



# Transformation Examples

- Algebraic Factoring ✓

$$F = \bar{A}\bar{C}\bar{D} + \bar{A}B\bar{C} + ABC + AC\bar{D} \quad G = \underline{16}$$

– Factoring:

$$F = \bar{A}(\bar{C}\bar{D} + B\bar{C}) + A(BC + C\bar{D}) \quad G = 16$$

– Factoring again:

$$F = \bar{A}\bar{C}(B + \bar{D}) + AC(B + \bar{D}) \quad G = \underline{12}$$


– Factoring again:

$$F = (\bar{A}\bar{C} + AC)(B + \bar{D}) \quad \underline{G} = 10$$



$$F = (\overline{A}C + AC)(B + \overline{D})$$

$2 + 2 + 2 + 2 + 2 = 10$  Cost

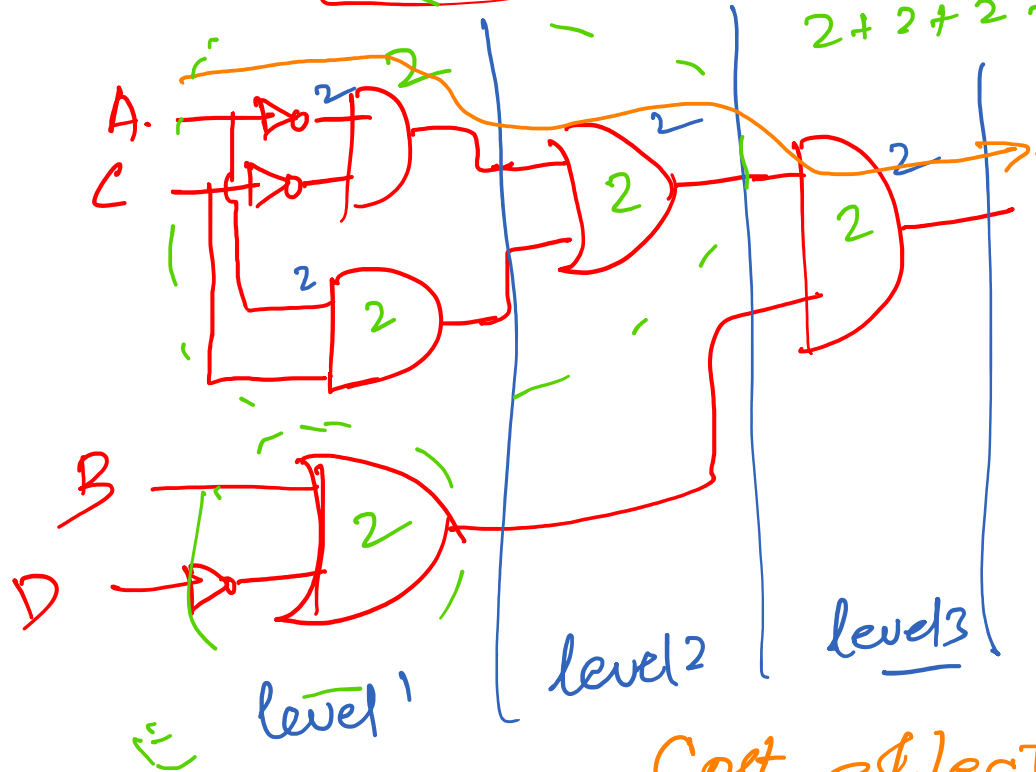

delay  
 $1 + 2 + 2 + 2 = 7$

Cost effective solution  
 may not be optimal for  
 performance.

# Transformation Examples

- Decomposition

- $F = A'C'D' + A'BC' + ABC + ACD'$      $G = 16$

- The terms  $A'C' + AC$  and  $B + D'$  can be defined as new functions  $H$  and  $E$  respectively, decomposing

- $F = (A'C' + AC)(B + D')$ :

- $F = H E, H = A'C' + AC, E = B + D' \quad G = 10$

- This series of transformations has reduced  $G$  from 16 to 10, a substantial savings.
- The resulting circuit has three levels plus input inverters.



# Transformation Examples

- Substitution of E into F

- Returning to F just before the final factoring step:

$$F = \bar{A}\bar{C}(B + \bar{D}) + AC(B + \bar{D}) \quad G = 12 \quad \checkmark$$

- Defining  $E = B + \bar{D}$ , and substituting in F:


$$F = \bar{A}\bar{C}E + ACE \quad G = 10$$

- This substitution has resulted in the same cost as the decomposition





# Transformation Examples

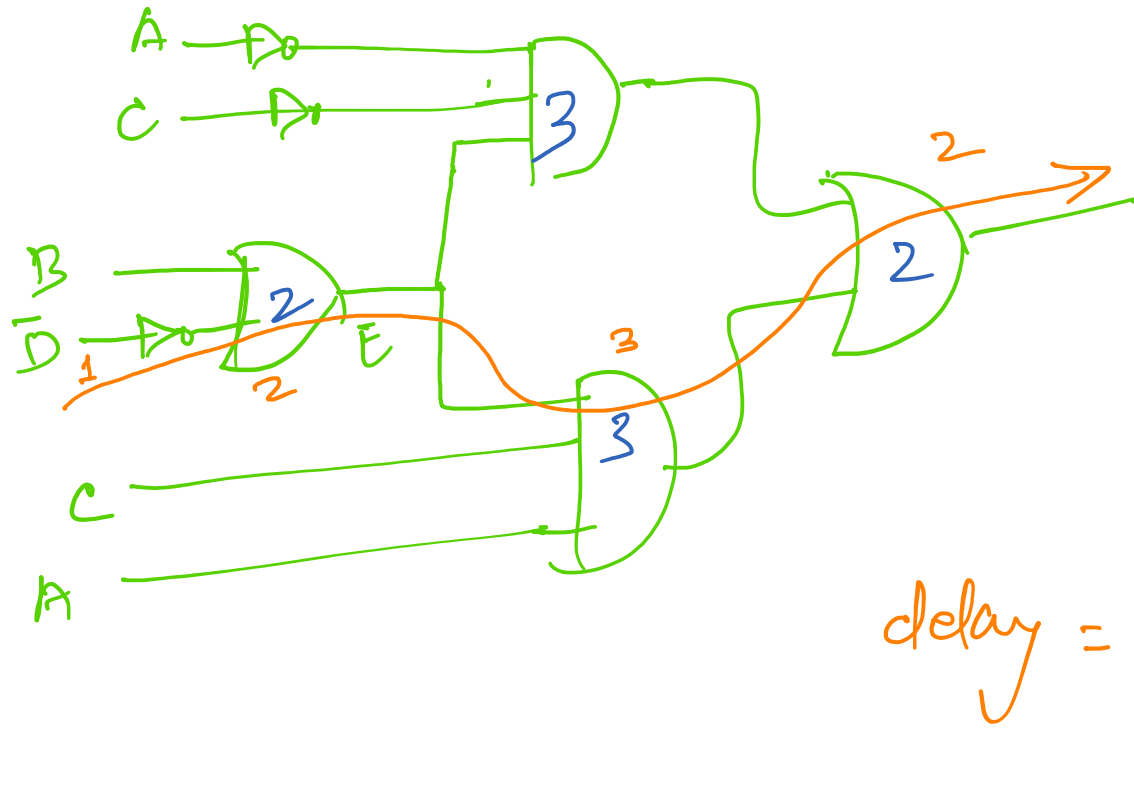

cost 10  
including inverts  
 $10 + 3 = 13$

$$\text{delay} = 1 + 2 + 3 + 2 = 8$$

# Summary

---

- Multi-level Optimization
- Transformations
  - Factoring - find a factored form from SOP or POS expression
  - Decomposition - express a function as a set of new functions
  - Substitution - express function  $F$  as a function of  $G$  and some or all of its original variables



# Thank You

