

Sequential Circuits

Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: viren@ee.iitb.ac.in

CS-226: Digital Logic Design



Lecture 21-A: 16 March 2021


CADSL

Serial Adder


STATE MACHINE

$$\begin{array}{r}
 c_{32} \ c_{31} \dots \ c_2 \ c_1 \ 0 \\
 a_{31} \dots \ a_2 \ a_1 \ a_0 \\
 + b_{31} \dots \ b_2 \ b_1 \ b_0 \\
 \hline
 s_{31} \dots \ s_2 \ s_1 \ s_0
 \end{array}$$

$c_1 =$

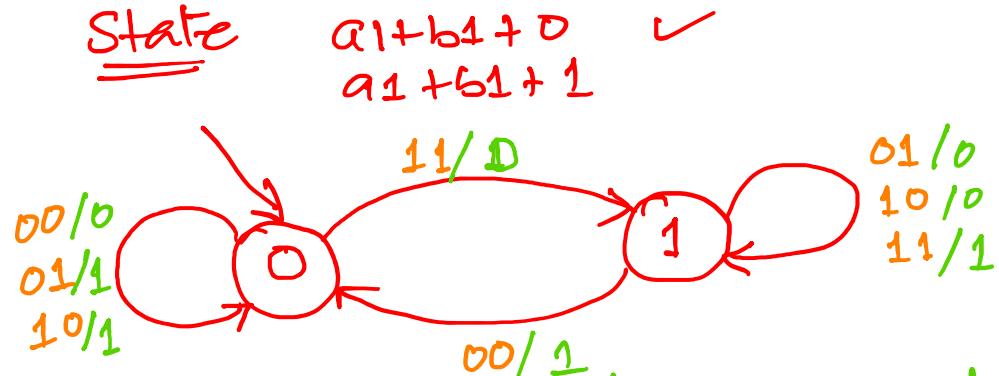

State transition diagram/stg

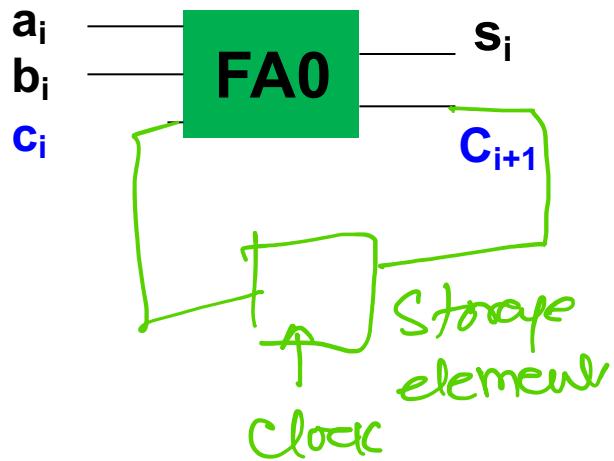

State	NS, Output			
	00	01	10	11
0	0	0	0	1
1	0	1	1	1

State transition table -



FINITE State Machine

$$M = (I, O, S, S_0, \delta, \lambda)$$

I : 8 input symbols
 $\{00, 01, 10, 11\}$


O : output symbol. $\{0, 1\}$

S : Set of states $\{0, 1\}$

S_0 : Initial state $\{0\}$

δ : $S \times I \rightarrow S$ [State transition function]

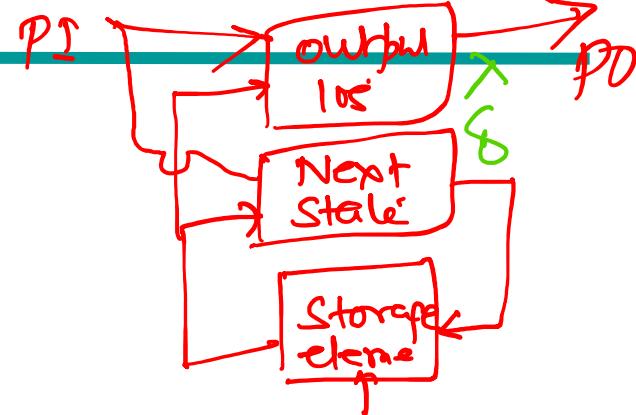λ : $S \times I \rightarrow O$ [Output function]



Design

① How many states
 $\log_2 |S|$


② How many storage elements

$$\log_2 |S|$$

- ③ δ
 ④ λ



State Machine

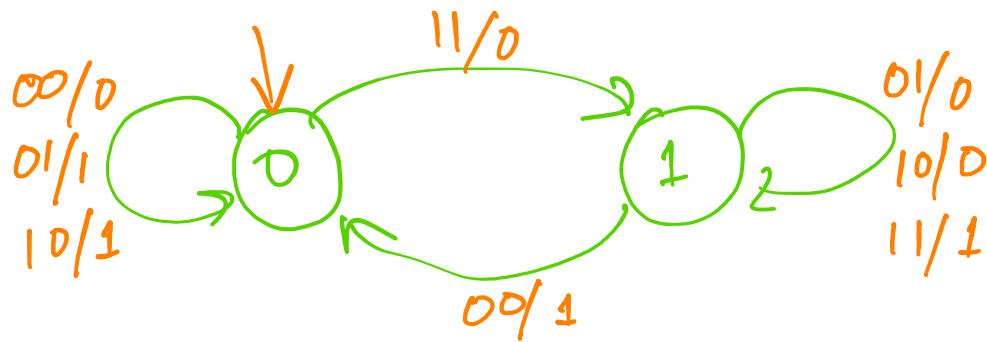


only 2 states
 $S = \{0, 1\}$ $|S| = 2$
 one storage element -
 $I = \{00, 01, 10, 11\}$
 $O = \{0, 1\}$

$$\delta: S \times I \rightarrow O$$


$$\delta(a, b, s)$$

$a \cdot b$	00	01	10	11
0	0	0	1	0
1	0	1	1	1
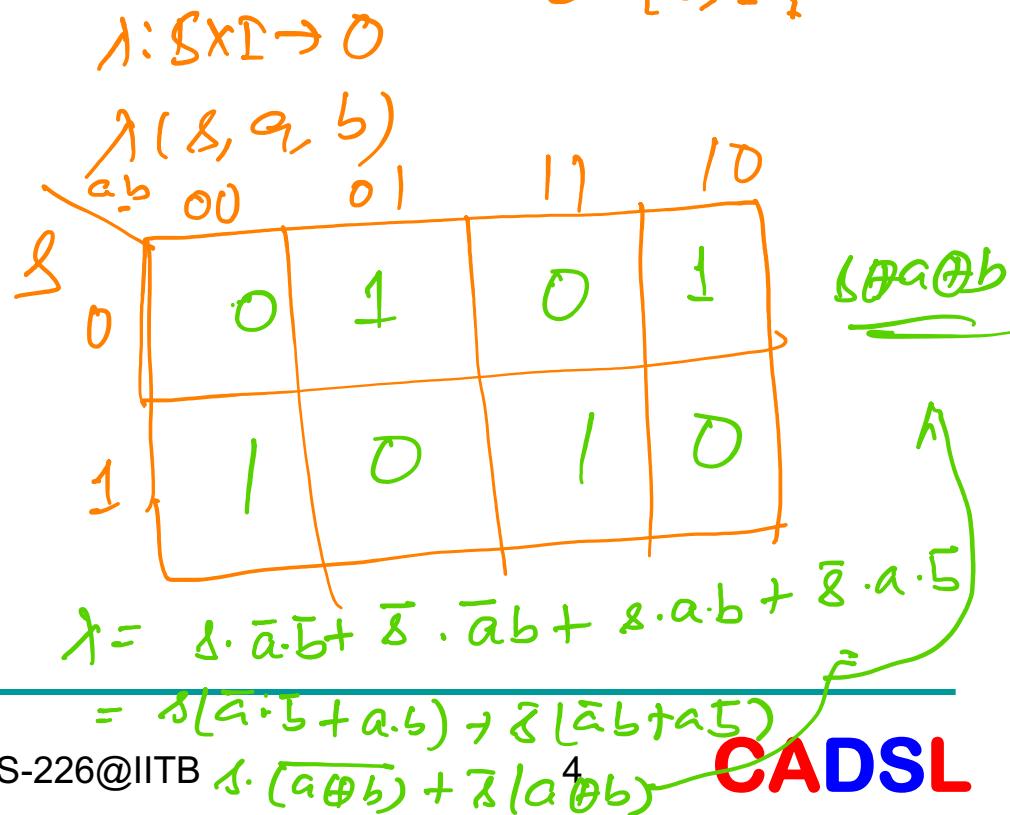
$$\delta(a, b, s) = a \cdot b + s \cdot b + s \cdot a$$




Finite State Machine

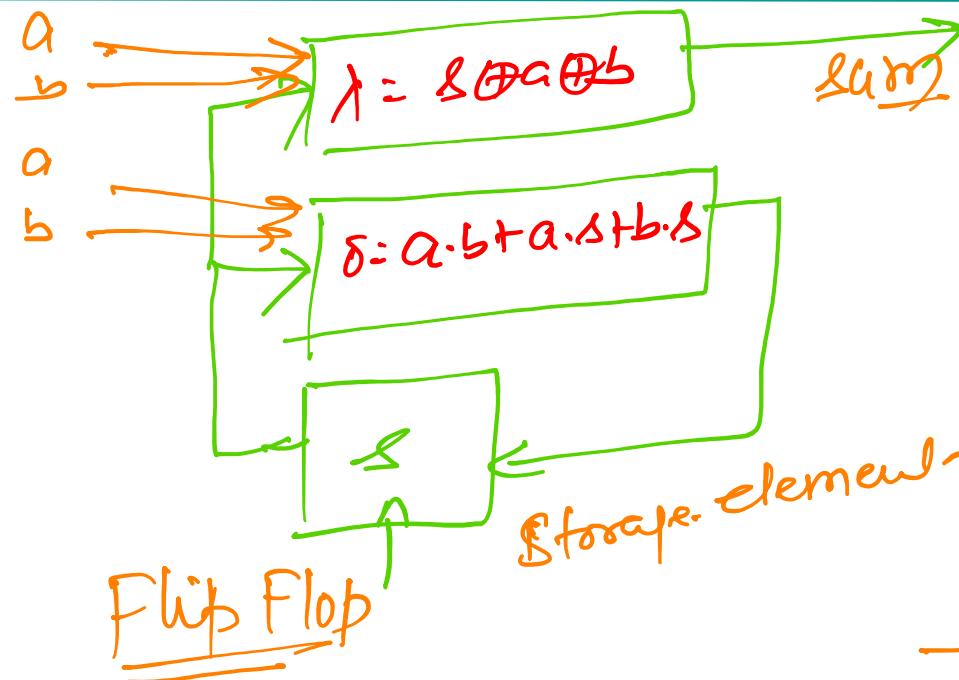

Synthesize λ
finite state

Storage. (FF)
1st
 λ

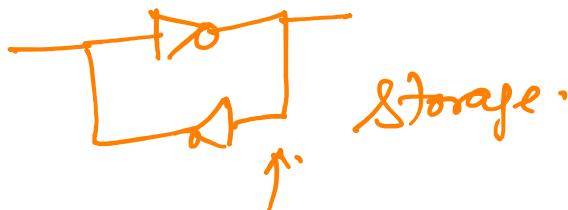


$$\begin{aligned}\delta(t+1) &= q(t) \cdot b(t) + q(t) \cdot \delta(t) + \\ \lambda(t+1) &= \delta(t) \oplus q(t) \oplus b(t)\end{aligned}$$



Finite State Machine

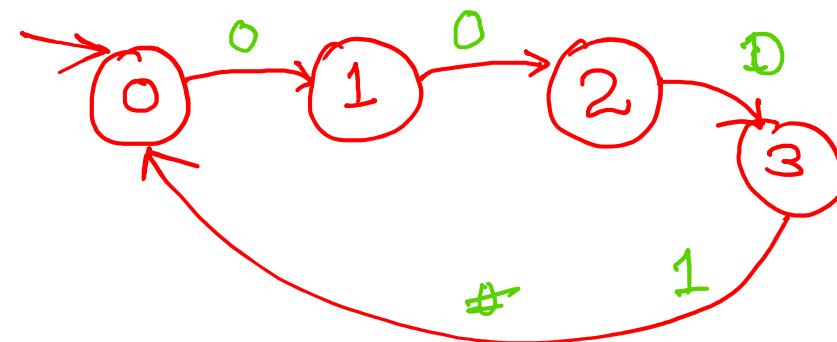0, 1, 2, 3, 0, 1, 2, 3, 0, 1, 2, 3, 0
0 0 0 1 0 0 0 1 0 0 ... 1



State transition diagram

$$\# \text{states} = |S| = 4$$

two state variable
 (s_1, s_0)


2 storage elements
(FP)

$$T = \emptyset \quad O = \{0, 1\}$$


? ? ! ?



Finite State Machine

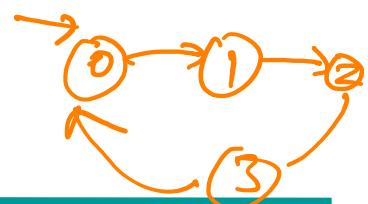


δ_1, δ_0

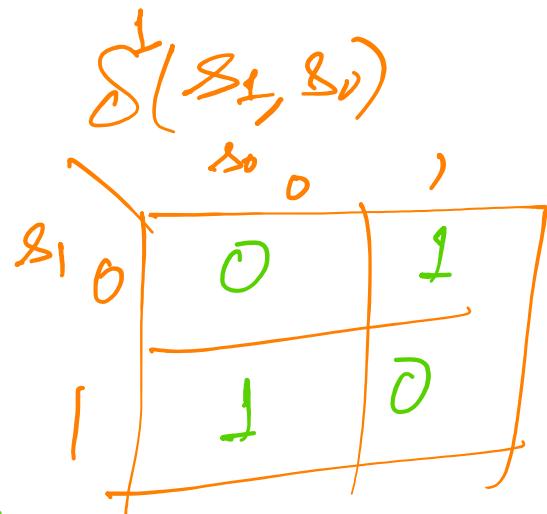

$$\begin{aligned}\delta^1 &= \delta_1 \bar{\delta}_0 + \bar{\delta}_1 \delta_0 \\ &= \delta_0 \oplus \delta_1\end{aligned}$$
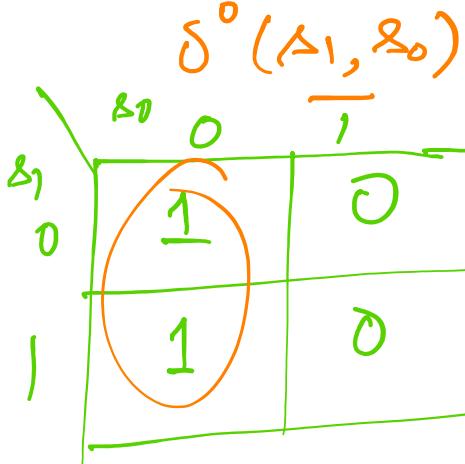
$$\begin{aligned}0 &\rightarrow \frac{\delta_1, \delta_0}{00} \\ 1 &\rightarrow 01 \\ 2 &\rightarrow 10 \\ 3 &\rightarrow 11\end{aligned}$$



$$\delta^0 = \bar{\delta}_0$$


$$\begin{aligned}\delta_1 &= \frac{\delta_1, \delta_0}{t_1, t_0} \\ t_1 &\leftarrow \text{next} \\ t_1(t) &\rightarrow \delta_1(\underline{t+})\end{aligned}$$

transition

δ_0	δ_1	t	$t+1$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0



Finite State Machine

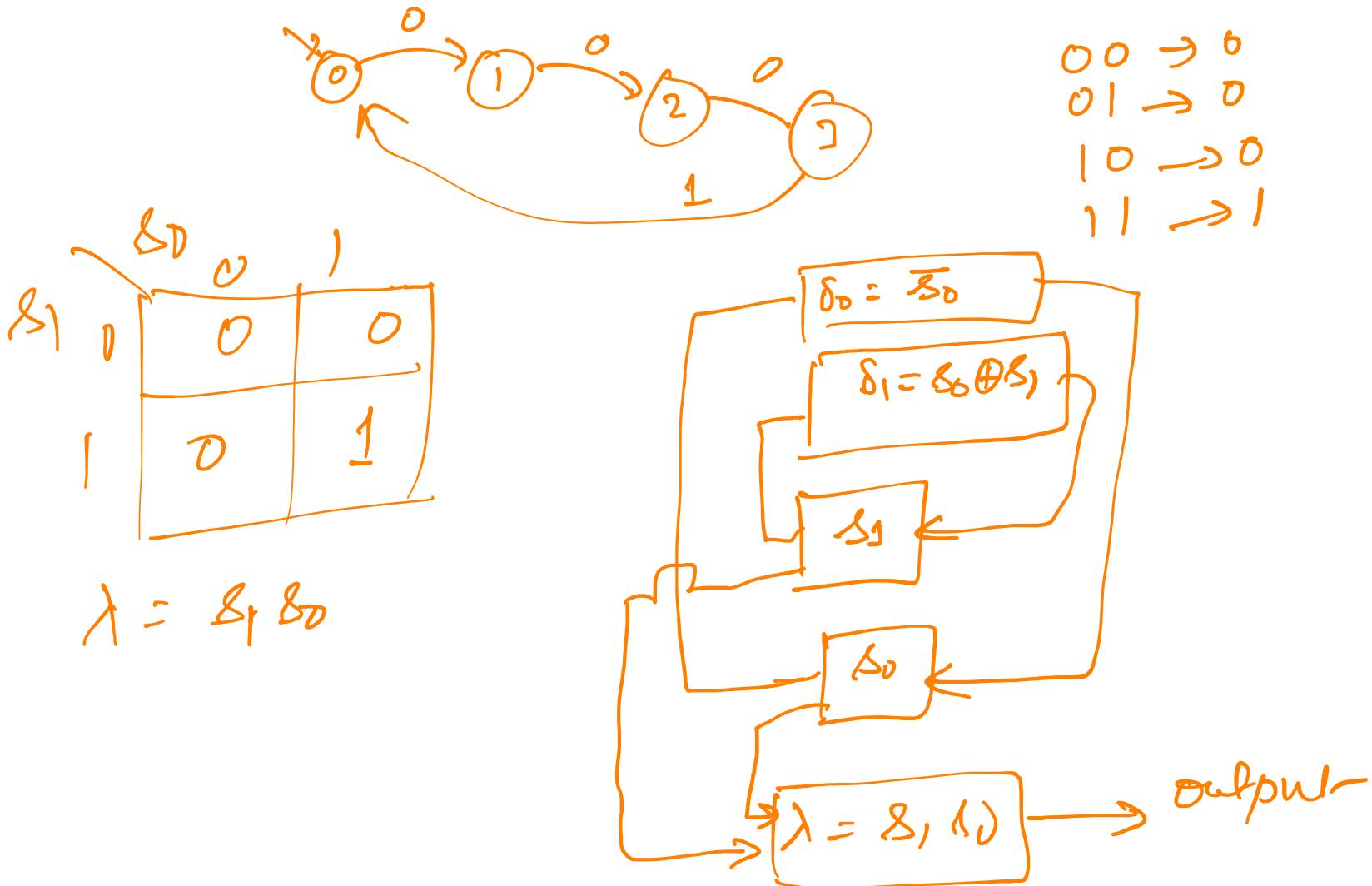

Finite State machine

d Construct state form

- Define states

- construct state transition graph

or S T T

- # storage elements $\log |S|$

- define encoding of states

- Compute δ, λ



Thank You

