

Sequential Circuits: State Minimization

Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: viren@ee.iitb.ac.in

CS-226: Digital Logic Design





Lecture 23: 30 March 2021

CADSL

Finite State Machine

$$M = (I, O, S, S_0, \delta, \lambda)$$

Vending Machine

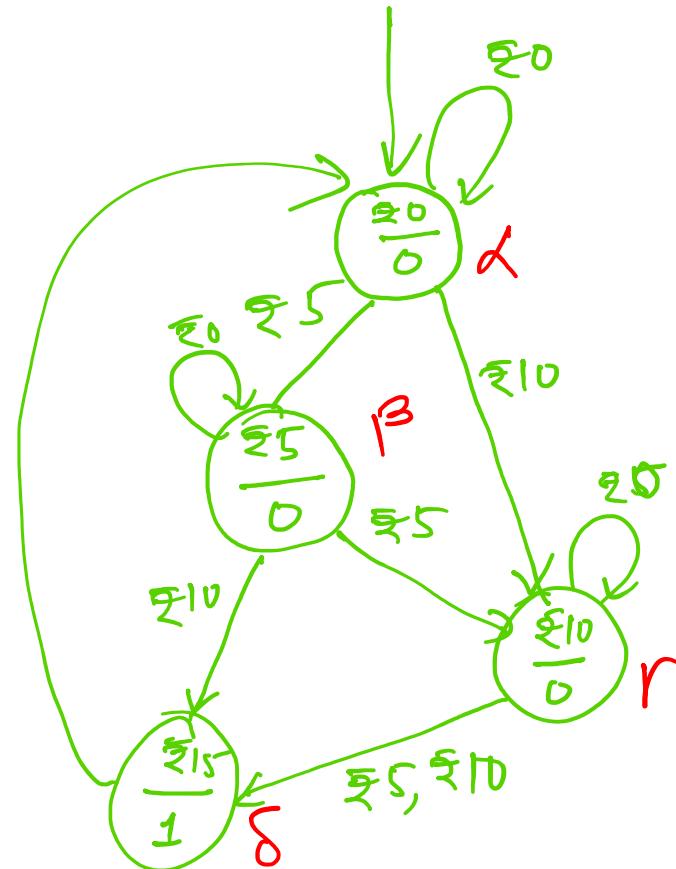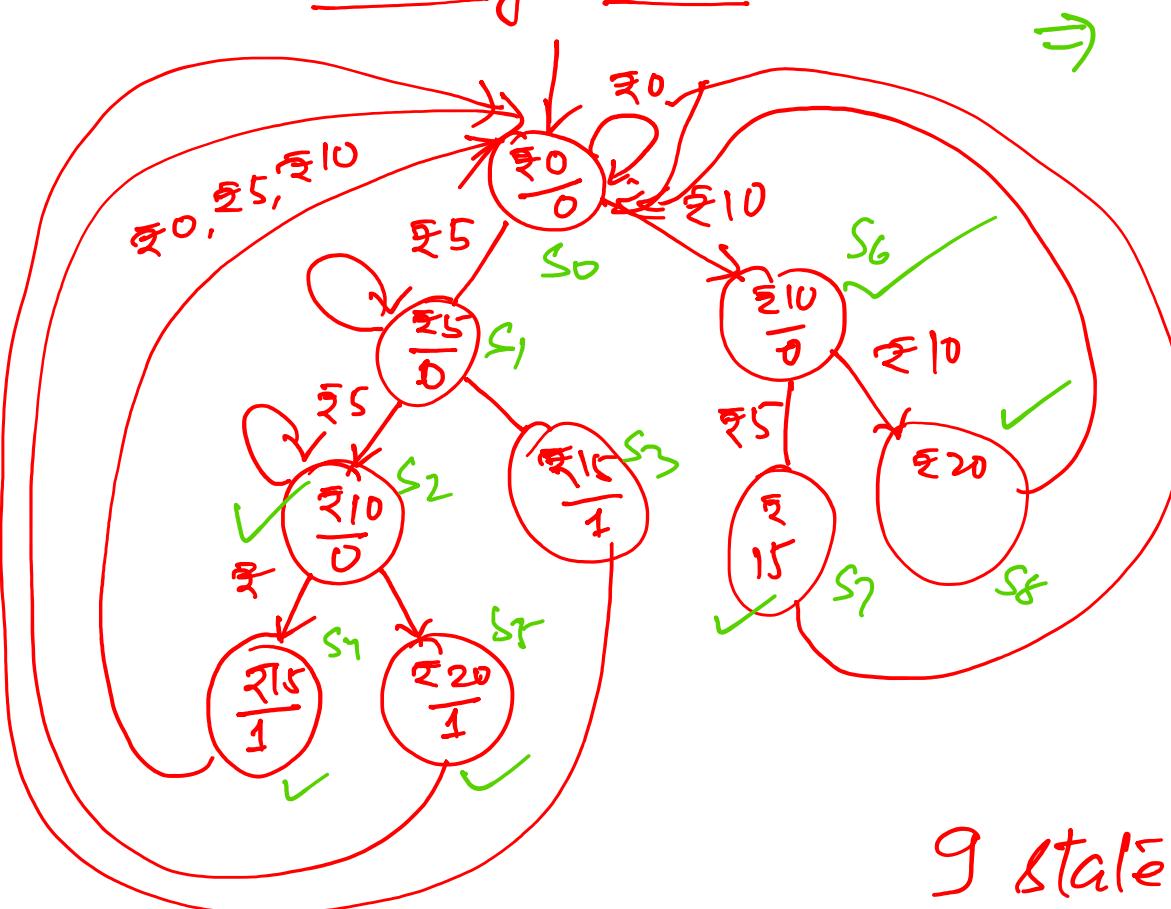

9 state \rightarrow 4 states

4 variable

2 variable

CADSL



State Minimization

X-Successor – If an input sequence X takes a machine from state S_i to state S_j , then S_j is said to be the X-successor of S_i

Strongly connected:- If for every pair of states (S_i, S_j) of a machine M there exists an input sequence which takes M from state S_i to S_j , then M is said to be strongly connected



State Equivalence

- Two states S_i and S_j of machine M are **distinguishable** if and only if there exists at least one finite input sequence which, when applied to M, causes different output sequences, depending on whether S_i or S_j is the initial state
- The sequence which distinguishes these states is called a **distinguishing** sequence of the pair (S_i, S_j)
- If there exists for pair (S_i, S_j) a distinguishing sequence of length k , the states in (S_i, S_j) are said to be **k-distinguishable**




State Equivalence

Machine M1

PS <u>z</u>	NS, z	
	X = 0	X = 1
A	E, 0	D, 1
B	F, 0	D, 0
C	E, 0	B, 1
D	F, 0	B, 0
E	C, 0	F, 1
F	B, 0	C, 0

(A, B) – 1 Distinguishable

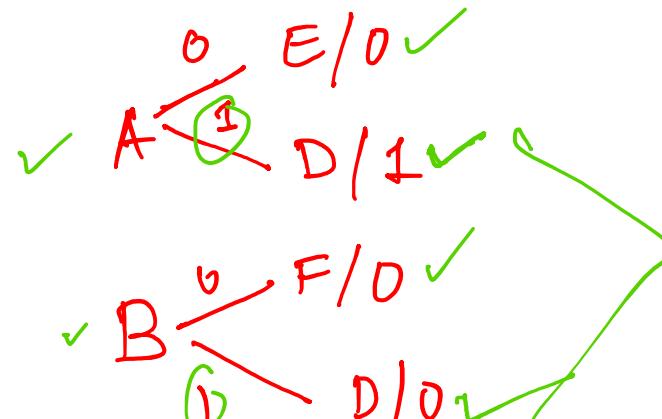

distinguishably

X = 1




State Equivalence

2- Indistinguishable.

Machine M1

PS	NS, z	
	X = 0	X = 1
A	E, 0	D, 1
B	F, 0	D, 0
C	E, 0	B, 1
D	F, 0	B, 0
E	C, 0	F, 1
F	B, 0	C, 0

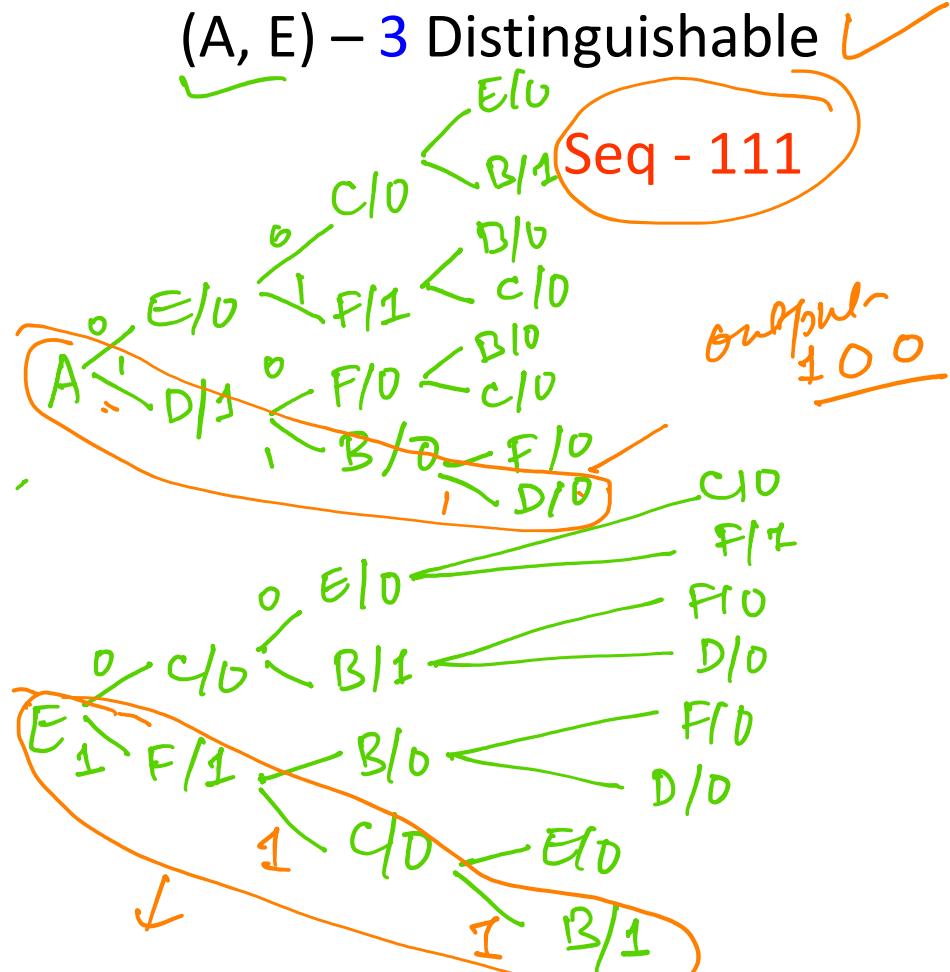

State Equivalence

Machine M1

PS	NS, z	
	X = 0	X = 1
A	E, 0	D, 1
B	F, 0	D, 0
C	E, 0	B, 1
D	F, 0	B, 0
E	C, 0	F, 1
F	B, 0	C, 0

(A, B) – 1 Distinguishable ✓

(A, E) – 3 Distinguishable ✓

2-equivalent Seq - 111
1-equivalent

k-equivalent – The states that are not k-distinguishable are said to be k-equivalent

Also r-equivalent r < k



Distinguishable States

K-distinguishable
K-1 equivalent



State Equivalence

- States S_i and S_j of machine M are said to be equivalent if and only if, for every possible input sequence, the same output sequence will be produced regardless of whether S_i or S_j is the initial state
 - States that are k-equivalent for all $k < n-1$, are equivalent
 - $S_i = S_j$, and $S_j = S_k$, then $S_i = S_k$
- (S_i, S_j, S_k)
equivalenzel^e set



State Equivalence

- The set of states of a machine M can be partitioned into disjoint subsets, known as equivalence classes
- Two states are in the same equivalence class if and only if they are equivalent, and are in different classes if and only if they are distinguishable

Property: If s_i and s_j are equivalent states, their corresponding X-successors, for all X, are also equivalent

s_p, s_q




State Minimization Procedure

1. Partition the states of M into subsets s.t. all states in same subset are 1-equivalent
2. Two states are 2-equivalent iff they are 1-equivalent and their l_i successors, for all possible l_i , are also 1-equivalent

(b) n

PS	NS, z	
	X = 0	X = 1
A	E, 0	D, 1
B	F, 0	D, 0
C	E, 0	B, 1
D	F, 0	B, 0
E	C, 0	F, 1
F	B, 0	C, 0

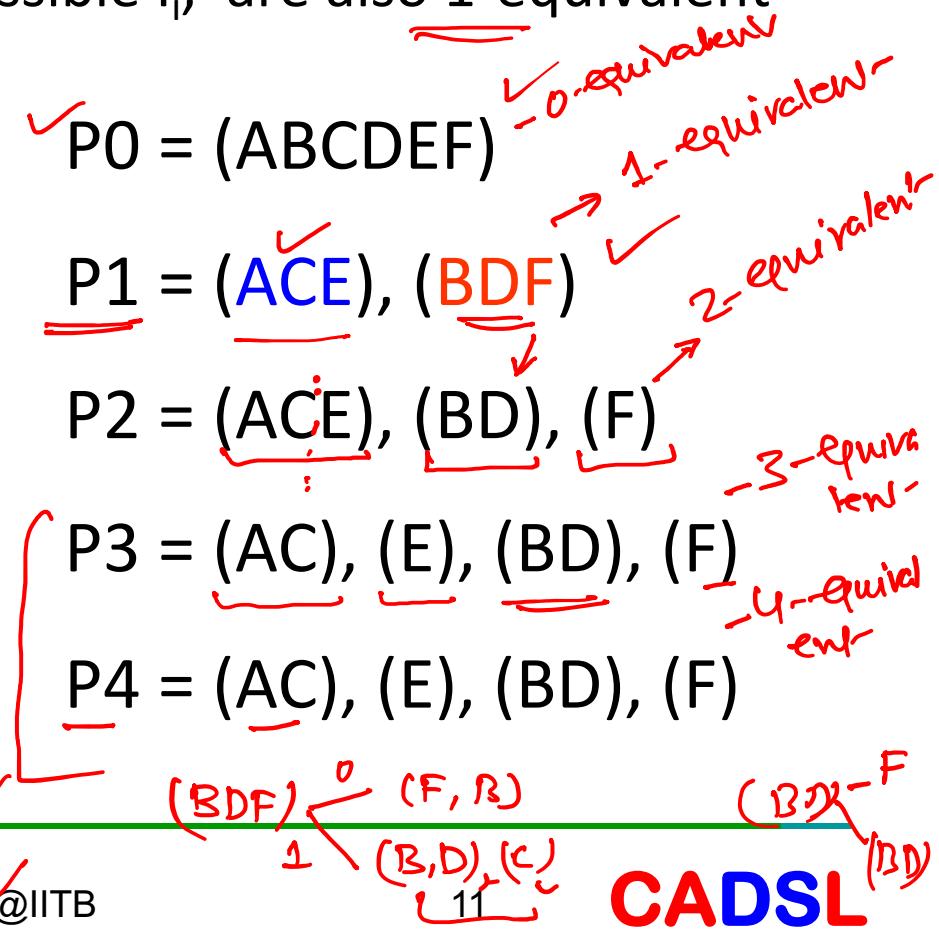

Machine Equivalence

- Two machines M1, M2 are said to be equivalent if and only if, for every state in M1, there is corresponding equivalent state in M2
- If one machine can be obtained from the other by relabeling its states they are said to be **isomorphic** to each other

PS	NS, z	
	X = 0	X = 1
AC - a ✓	$\beta, 0$	$\gamma, 1$
E - β ✓	$\alpha, 0$	$\delta, 1$
BD - γ ✓	$\delta, 0$	$\gamma, 0$
F - δ ✓	$\gamma, 0$	$\alpha, 0$



State Equivalence - Example

Machine M2

PS	NS, z	
	X = 0	X = 1
A	E, 0	C, 0
B	C, 0	A, 0
C	B, 0	G, 0
D	G, 0	A, 0
E	F, 1	B, 0
F	E, 0	D, 0
G	D, 0	G, 0

$P_0 = (ABCDEFG)$ ✓
 $P_1 = (\underline{ABCDFG}) (\underline{E})$ ✓
 $P_2 = (\underline{\underline{AF}}) (\underline{BCDG}) (\underline{E})$ ✓
 $P_3 = (\underline{\underline{AF}}) (\underline{BD}) (\underline{CG}) (\underline{E})$ ✓
 $P_4 = (\underline{A}) (\underline{F}) (\underline{BD}) (\underline{CG}) (\underline{E})$]
 $P_5 = (A) (F) (BD) (CG) (E)$]



Finite State Machine

K-equivalence classes

If successors are also K-equivalent

then states are (K+1) equivalent

Partition two states until

- get no more partition
- n times



state machine



Thank You



30 Mar 2021

CS-226@IITB

15

CADSL