

# Sequential Circuits: Verification

---

Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: [viren@ee.iitb.ac.in](mailto:viren@ee.iitb.ac.in)

*CS-226: Digital Logic Design*


---



Lecture 27: 08 April 2021



**CADSL**

# Finite State Machine

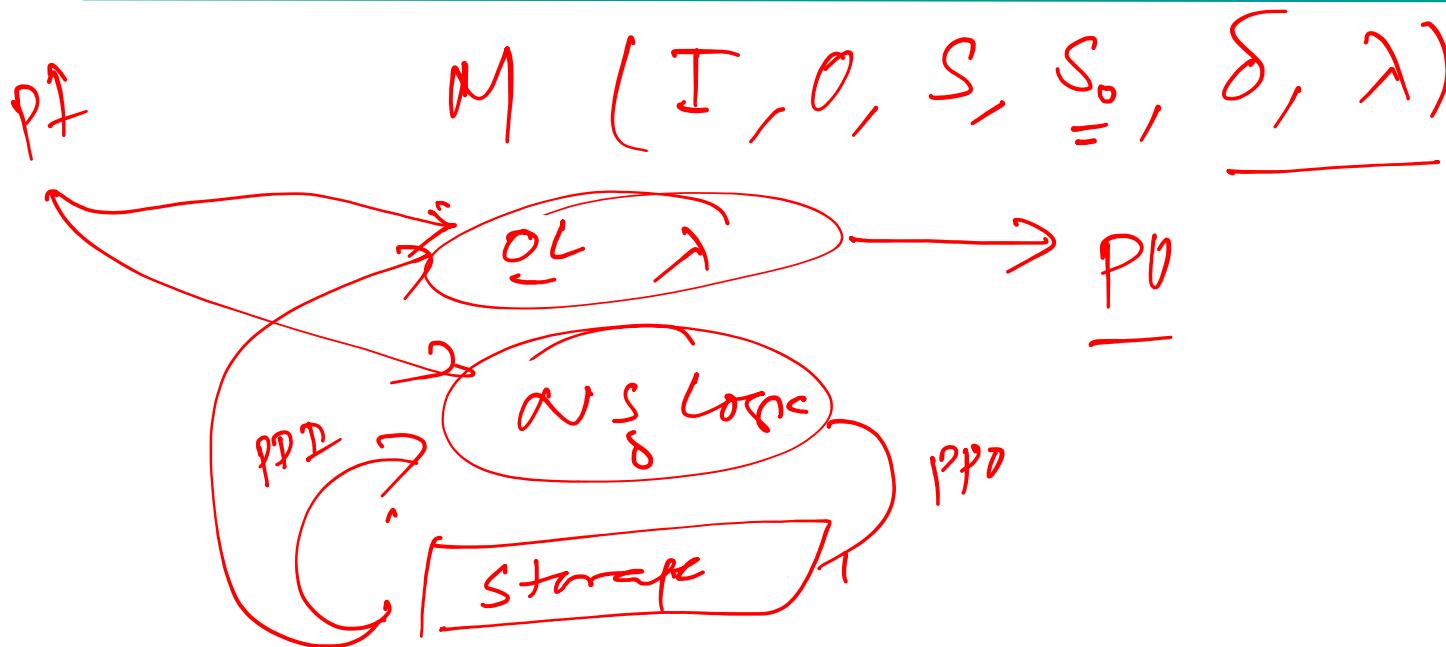


# Reachability-Based Equivalence Checking
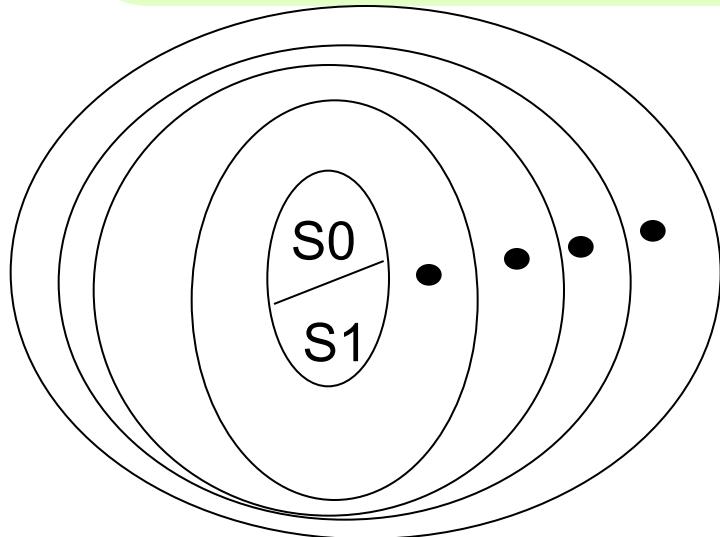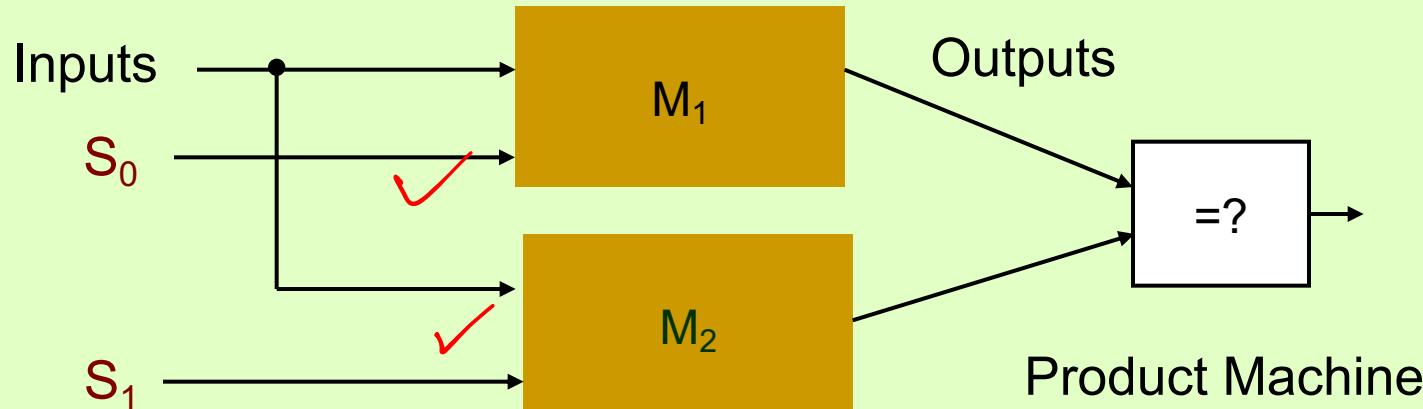
## Approach 3: Symbolic Traversal Based Reachability Analysis




- Build product machine of  $M_1$  and  $M_2$
- Traverse state-space of product machine starting from reset states  $(S_0, S_1)$
- Test equivalence of outputs in each state
- Can use any state-space traversal technique

# Forward Reachability


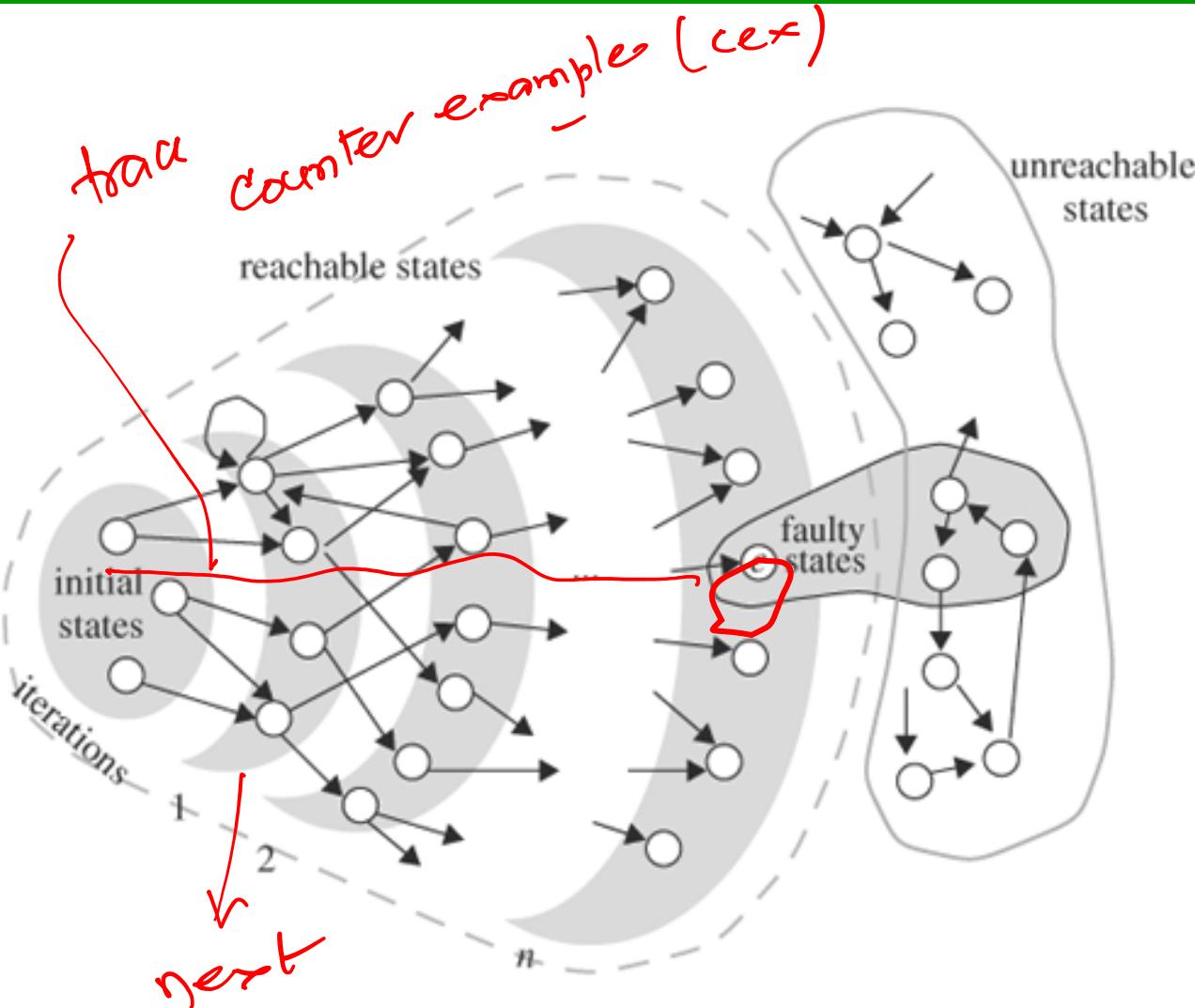

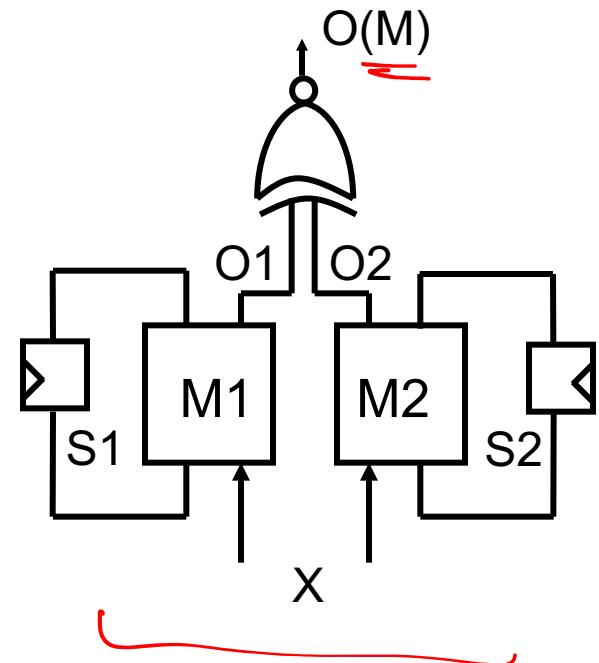
# Sequential Verification

- Symbolic FSM traversal of the product machine
- Given two FSMs:  $M_1(X, S_1, \delta_1, \lambda_1, O_1)$ ,  $M_2(X, S_2, \delta_2, \lambda_2, O_2)$
- Create a product FSM:  $M = M_1 \times M_2$ 
  - traverse the states of  $M$  and check its output for each transition
  - the output  $O(M) = 1$ , if outputs  $O_1 = O_2$
  - if all outputs of  $M$  are 1,  $M_1$  and  $M_2$  are *equivalent*
  - otherwise, an *error state* is reached
  - *error trace* is produced to show:  $M_1 \neq M_2$



# FSM Traversal in Action

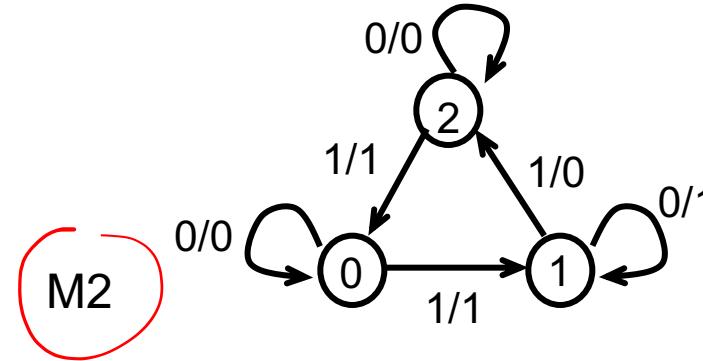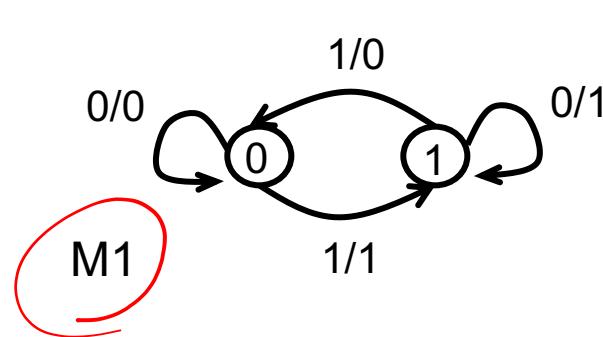


Initial states:  $s_1=0, s_2=0, s=(0.0)$

State reached	$Out(M)$
$x=0 \ x=1$	

- New  $^0 = (0.0) \quad 1 \quad 1$
- New  $^1 = (1.1) \quad 1 \quad 1$
- New  $^2 = (0.2) \quad 1 \quad 1$
- New  $^3 = (1.0) \quad 0 \quad 0$

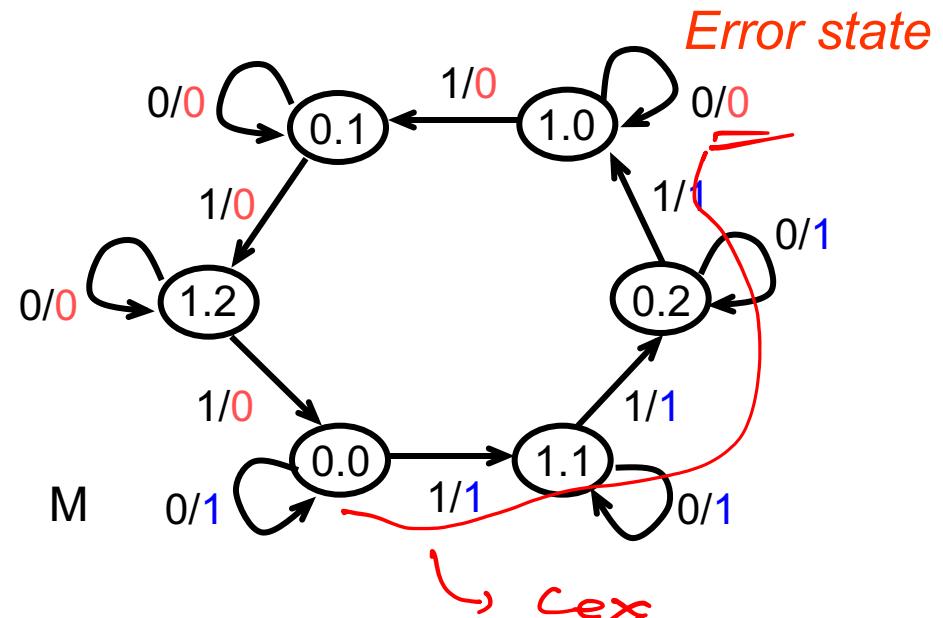- STOP - backtrack to initial state to get *error trace*:  $x=\{1,1,1,0\}$



# FSM Traversal - Algorithm

---

- Traverse the product machine  $M(X, S, S_0, \delta, \lambda, O)$ 
  - start at an initial state  $S_0$
  - iteratively compute symbolic image  $\text{Img}(S_0, R)$  (set of *next states*):

$$\text{Img}(S_0, R) = \exists_x \exists_s S_0(s). R(\underline{x}, \underline{s}, \underline{t})$$

$$R = \prod_i R_i = \prod_i (t_i \equiv \delta_i(s, x))$$

until an *error state* is reached

- transition relation  $R_i$  for each next state variable  $t_i$  can be computed as  $t_i = \underline{(t \otimes \delta(s, x))}$   
(this is an alternative way to compute transition relation, when design is specified at gate level)



# How to Represent TF ?


---

- ❖ Given a deterministic transition function  $(s,x)$  the corresponding transition relation is defined by
  - $T(s,x,t) = \prod(t_i = \delta_i(s,x))$
- ❖  $T(s,x,t) = 1$  denotes a set of encoded triples  $(s,x,t)$ , each representing a transition in the FST of a given FSM
- ❖ Straight forward to compute image
- ❖ Need new boolean operation
  - Existential Abstraction
  - $\exists_{xi}.f = f_{xi} + f_{\bar{xi}}$
  - $f_{xi}$ - smallest (fewest minterm) function that contains all minterms of  $f$  and independent of  $xi$


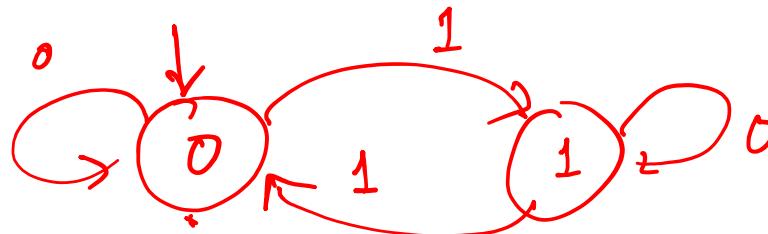
# How to Traverse?

$$\begin{array}{l} x, \delta \\ \hline S = \{0, 1\} \\ \textcircled{0} \quad \textcircled{1} \end{array}$$



$x \cdot 0$	0	1
0	0	1..
1	1	0

$$\delta = \bar{\delta}x + \delta \bar{x}$$

$$R(\cancel{x}, x, t) = (t = \delta)^\vee$$

$$R = (t = \bar{x}x + x\bar{x}) = (t \odot (\bar{x}x + x\bar{x}))$$

$$= t \cdot (\bar{x}x + x\bar{x}) + \bar{t} (\overline{\bar{x}x + x\bar{x}})$$

$$= t\bar{x}x + t x\bar{x} + \bar{t} (\overline{\bar{x}x} \cdot \overline{x\bar{x}})$$

$$= t\bar{x}x + t x\bar{x} + \bar{t} ((\bar{x}+x) \cdot (\bar{x}+x))$$

$$= t\bar{x}x + t x\bar{x} + \bar{t} \bar{x}\bar{x} + \bar{t} x x.$$



# How to Traverse?

$$R(q, s, t) = \frac{t \bar{x}x + t \bar{s}\bar{x} + \bar{t} \bar{x}\bar{x} + \bar{t} s x}{\text{initial } 0 \quad \text{at } \bar{s}}$$

$$f(x, s, t) = (t \bar{x}x + t \bar{s}\bar{x} + \bar{t} \bar{x}\bar{x} + \bar{t} s x) \cdot \bar{s}$$

$$f(\overset{\checkmark}{x}, s, t) = t \bar{x}x + \bar{t} \bar{x}\bar{x}$$

$$f_x = t \bar{x}$$

$$f_{\bar{x}} = \bar{t} \bar{x}$$

$$f(s, t) = t \bar{x} + \bar{t} \bar{x} = \bar{x}$$

$$f(1, t) = \bar{x}$$

$$\begin{aligned} f_x &= 0 \\ f_{\bar{x}} &= 1 \\ f(t) &= 0 + 1 = \underline{\underline{1}} \\ &\text{Σ} 0, 13. \end{aligned}$$



# How to Represent TF ?

---

- ❖ Given  $f(s, x) = f(s, \dots s_n, x_1, \dots x_m)$  the existential abstraction w.r.t a set of variables is defined as



$$\exists_x . f(s, x) = \exists_{x_1} (\exists_{x_2} (\dots \exists_{x_m} (f(s, x))))$$


## ❖ Procedure

$$\lambda = \underline{x_1, \dots, x_m}$$


- Compute TF,  $f(s, x, t)$
- Compute conjunction of R and C
- Existentially abstract all s variable and all x variable - provides  $f(t)$
- $f(t)$  is the smallest function independent of s and x which contains all the triples in  $f(s, x, t)$



# State Reachability in Product FSM

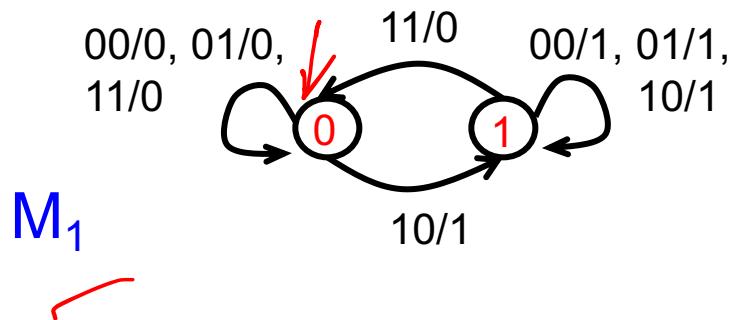

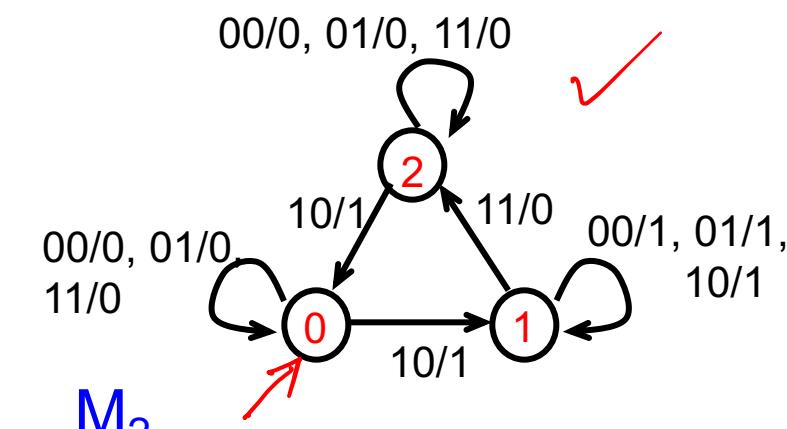
- $t_1 = \delta_{\text{1}}^{\text{1}} = x_1 x_2' + s_1 x'_1$
- $\lambda^1 = \delta_{\text{1}}^{\text{1}}$




- 0=00, 1=01, 2=10
- $t_2 = \delta_{\text{2}}^{\text{2}} = s_3 x_1 x_2 + s_2 (x'_1 + x_2)$
- $t_3 = \delta_{\text{3}}^{\text{2}} = s'_2 x_1 x'_2 + s_3 x'_1$
- $\lambda^2 = s_3 x'_1 + x_1 x'_2$
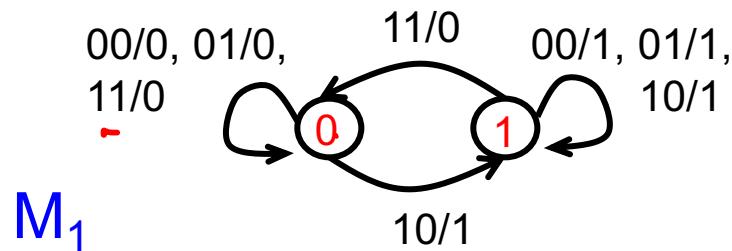
# State Reachability in Product FSM


$\underline{x_1} \underline{x_2}$   
 $\delta_1$



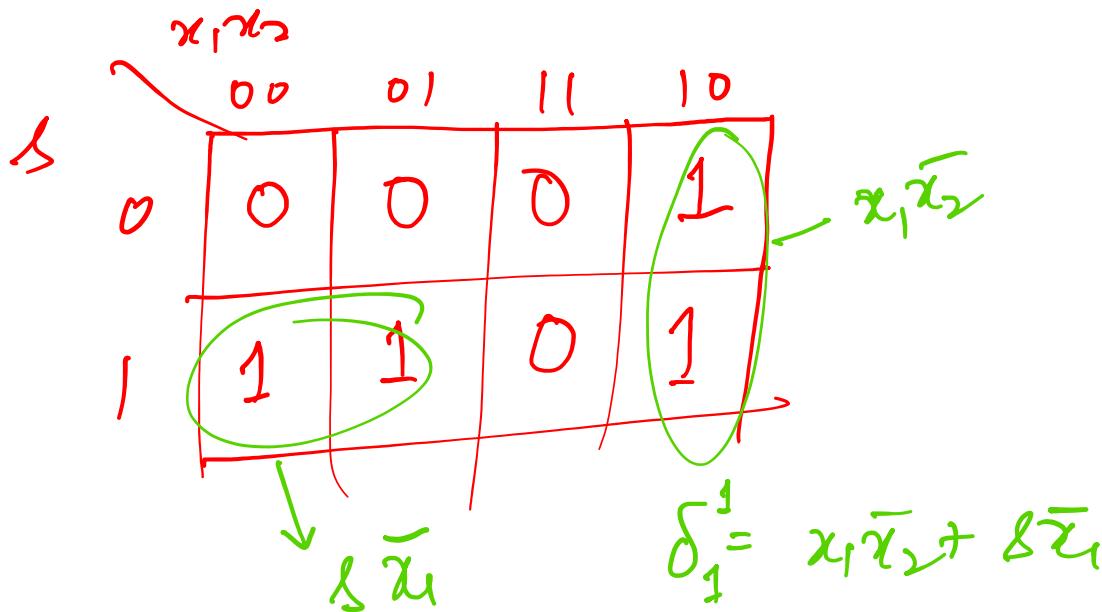- $t_1 = \delta_{\underline{1}}^{\underline{1}} = x_1 x_2' + s_1 \cdot x_1'$  ✓
- $\lambda^1 = \delta_{\underline{1}}^{\underline{1}} = x_1 \bar{x}_2 + \delta_1 \bar{x}_1$



# State Reachability in Product FSM

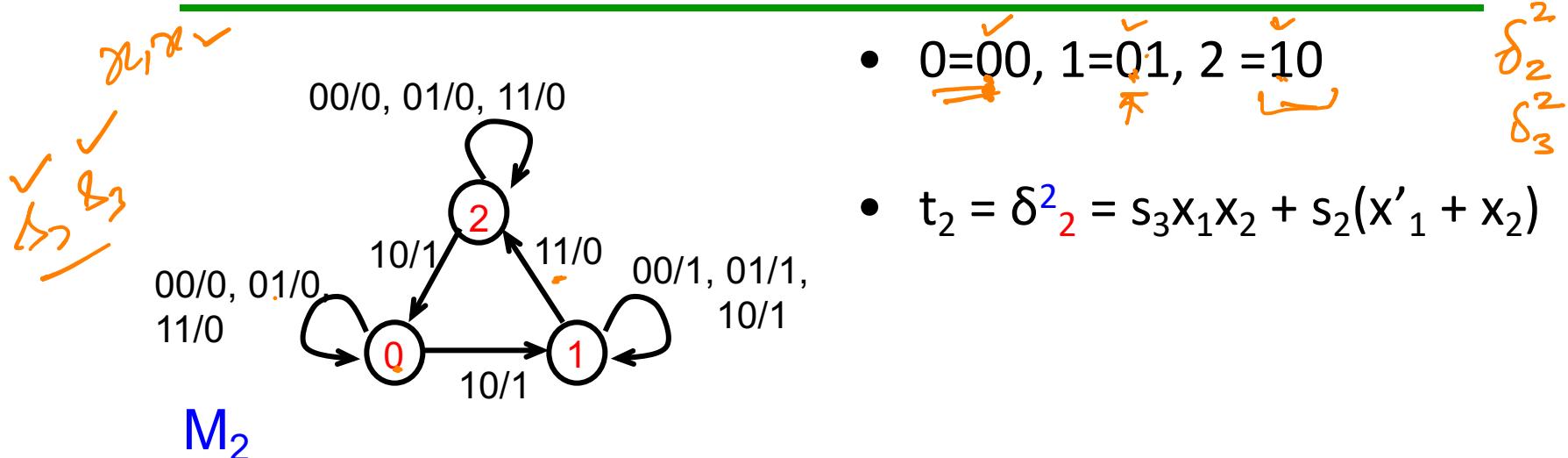

$$0 = \underline{\underline{00}}, 1 = \underline{01}, 2 = \underline{10}$$

$$t_2 = \delta_2^2 = s_3 x_1 x_2 + s_2 (x'_1 + x_2)$$

Karnaugh Map for State 2 Reachability:



	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	1	1	1	0

Annotations on the Karnaugh Map:

- Row 00:  $\delta_2 x_2$
- Row 01:  $\delta_2 x_2$
- Column 11:  $\delta_3 x_3$
- Column 10:  $\delta_2 x_2$
- Column 00:  $\delta_2 x_2$
- Column 01:  $\delta_2 x_2$
- Column 11:  $\delta_2 x_2$
- Column 10:  $\delta_2 x_2$

$$\delta_2^2 = \delta_3 \bar{x}_1 + \delta_2 x_2 + \underline{\delta_3 x_1 x_2}$$

# State Reachability in Product FSM

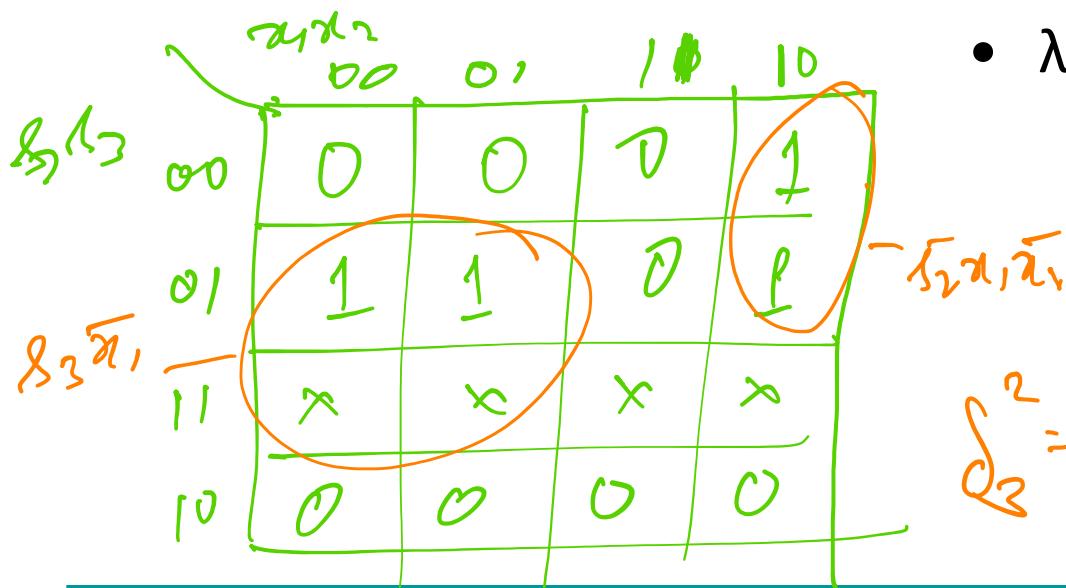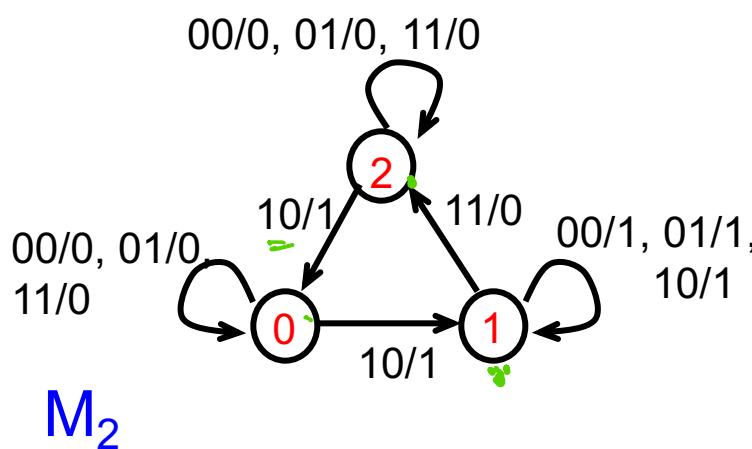


- $0=00, 1=01, 2=10$
- $t_2 = \delta_2^2 = s_3 x_1 x_2 + s_2(x'_1 + x_2)$
- $t_3 = \delta_3^2 = s'_2 x_1 x'_2 + s_3 x'_1$
- $\lambda^2 = s_3 x'_1 + x_1 x'_2$

$$\delta_2^2 = \delta_3 \bar{x}_2 + \delta_2 \bar{x}_1$$


# State Reachability in Product FSM

---

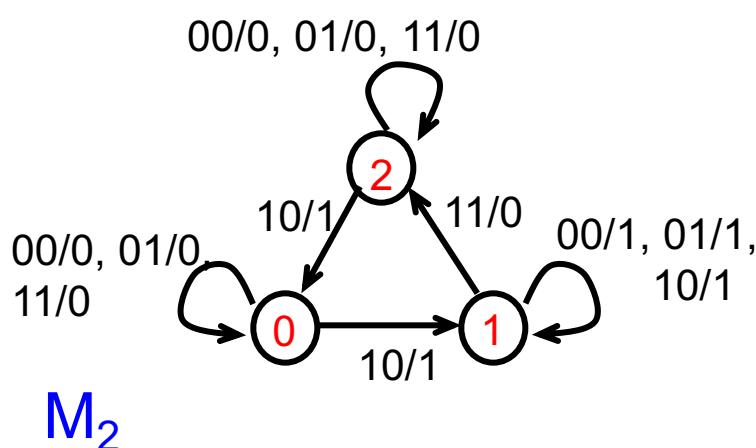


- $0=00, 1=01, 2=10$
- $\lambda^2 = s_3x'_1 + x_1x'_2$

# State Reachability in Product FSM

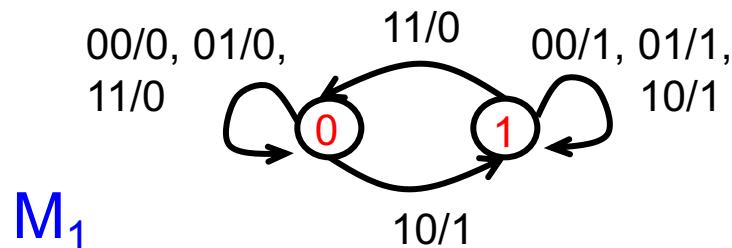

- $t_1 = \delta_1^1 = x_1 x_2' + s_1 x'_1$
- $\lambda^1 = \delta_1^1$

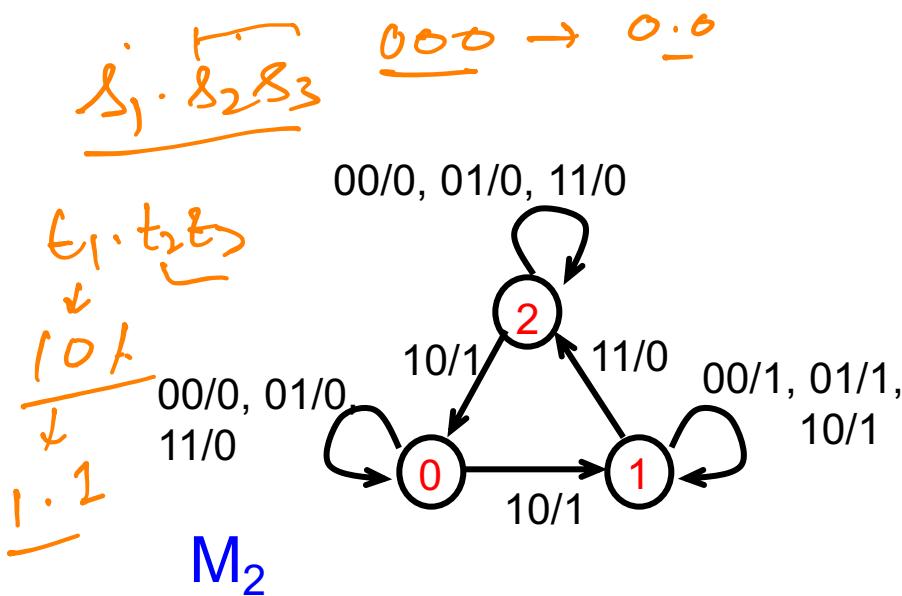$\delta_1^1$   $\delta_2^1$   $\delta_3^1$   
 $\delta_1^2$   $\delta_2^2$   $\delta_3^2$   
 $\delta_1^3$   $\delta_2^3$   $\delta_3^3$



- $0=00, 1=01, 2=10$
- $t_2 = \delta_2^2 = s_3 x_1 x_2 + s_2 (x'_1 + x_2)$
- $t_3 = \delta_3^2 = s'_2 x_1 x'_2 + s_3 x'_1$
- $\lambda^2 = s_3 x'_1 + x_1 x'_2$



# Symbolic FSM Traversal

---

Transition relation of the product machine

❖  $\text{R}(s, x, t) = (t_1 \equiv \delta_1^1). (t_2 \equiv \delta_2^2). (t_3 \equiv \delta_3^3)$

$$T(s, x, t) = (t_1 \equiv x_1 x_2' + s_1 x_1'). (t_2 \equiv s_3 x_1 x_2 + s_2(x_1' + x_2)). (t_3 \equiv s_2' x_1 x_2' + s_3 x_1')$$

The diagram illustrates the mapping between the terms in the equation  $R(s, x, t)$  and the terms in the equation  $T(s, x, t)$ . Orange arrows connect the terms: one arrow points from  $t_1 \equiv \delta_1^1$  to  $x_1 x_2' + s_1 x_1'$ ; another points from  $t_2 \equiv \delta_2^2$  to  $s_3 x_1 x_2 + s_2(x_1' + x_2)$ ; and a third points from  $t_3 \equiv \delta_3^3$  to  $s_2' x_1 x_2' + s_3 x_1'$ .



# Symbolic FSM Traversal

---

Transition relation of the product machine

- ❖  $T(s, x, t) = (t_1 \equiv \delta_1^1). (t_2 \equiv \delta_2^2). (t_3 \equiv \delta_3^3)$
- ❖ Initial State is  $s'_1 s'_2 s'_3$
- ❖  $T(s, x, t). C(s) = T(s, x, t). s'_1 s'_2 s'_3$   
 $= (t_1 \equiv s'_1 x_1 x_2). (t_2 \equiv 0). (t_3 \equiv s'_2 x_1 x'_2). s'_1 s'_2 s'_3$

$$f(s, x, t) = (t_1 \equiv x_1 x'_2 + s_1 x'_1). (t_2 \equiv s_3 x_1 x_2 + s_2(x'_1 + x_2)). (t_3 \equiv s'_2 x_1 x'_2 + s_3 x'_1) . s'_1 s'_2 s'_3$$

- Since this conjunction evaluate to 1 for just one s-minterm  $(s'_1 s'_2 s'_3)$



# Symbolic FSM Traversal

Transition relation of the product machine

- ❖  $T(s, x, t) = (t_1 \equiv \delta_1^1). (t_2 \equiv \delta_2^2). (t_3 \equiv \delta_3^3)$
- ❖ Initial State is  $s'_1 s'_2 s'_3$

$$T(s, x, t) = (t_1 \equiv x_1 x'_2 + s_1 x'_1). (t_2 \equiv s_3 x_1 x_2 + s_2 (x'_1 + x_2)). (t_3 \equiv s'_2 x_1 x'_2 + s_3 x'_1) \cdot s'_1 s'_2 s'_3$$

$$\begin{aligned} G(x, t) &= \exists_s (T(s, x, t). C(s)) && (t_1 \equiv \text{min}) (t_2 = 0) (t_3 \equiv \text{max}) \\ &= (t_1 \equiv x_1 x'_2). (t_2 \equiv 0). (t_3 \equiv x_1 x'_2) && \exists_s f(x, s, t) \end{aligned}$$



# Symbolic FSM Traversal


$$\begin{aligned}
 G(x,t) &= \exists_s (T(s,x,t).C(s)) \\
 &= (t_1 \equiv x_1 x'_2) \cdot (t_2 \equiv 0) \cdot (t_3 \equiv x_1 x'_2)
 \end{aligned}$$

- Since this conjunction evaluate to 1 for just one s-minterm ( $s'_1 s'_2 s'_3$ )

$$g_{x_1 x'_2} = (t_1 \equiv 1) \cdot (t_2 \equiv 0) \cdot (t_3 \equiv 1)$$

$$g_{x'_1 x_2} = g_{x'_1 x'_2} = g_{x_1 x_2} = (t_1 \equiv 0) \cdot (t_2 \equiv 0) \cdot (t_3 \equiv 0)$$
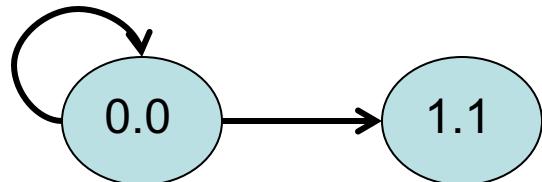
$$\text{Img}(T,C) = g(x,t) = t'_1 t'_2 t'_3 + t_1 t'_2 t_3$$



$$C_{new}(s) = C_{old}(s)$$

$t_1$	$t_2$	$t_3$	
00	0	0	0
01	0	0	0
10	1	0	1
11	0	0	0

$$\begin{aligned}
 C(s) &= \overline{s_1} \overline{s_2} \overline{s_3} + \overline{s_1} \overline{s_2} s_3 + s_1 \overline{s_2} \overline{s_3} + s_1 \overline{s_2} s_3 + s_1 s_2 \overline{s_3} + s_1 s_2 s_3 \\
 C_{new}(s) &= \overline{s_1} \overline{s_2} \overline{s_3} + s_1 \overline{s_2} \overline{s_3} + s_1 s_2 \overline{s_3} + s_1 s_2 s_3
 \end{aligned}$$


$$\begin{aligned}
 \lambda &= \lambda_1 \oplus \lambda_2 + \overline{s_2} (\overline{s_1} \overline{s_3} + s_1 \overline{s_3}) \\
 &= \lambda_1 \oplus \lambda_2 + \overline{s_2} \overline{s_1} \overline{s_3} + \overline{s_2} s_1 \overline{s_3}
 \end{aligned}$$

$0,1 \{ 0,1 \}$

# Forward Reachability

- BDD is used

ROBDD

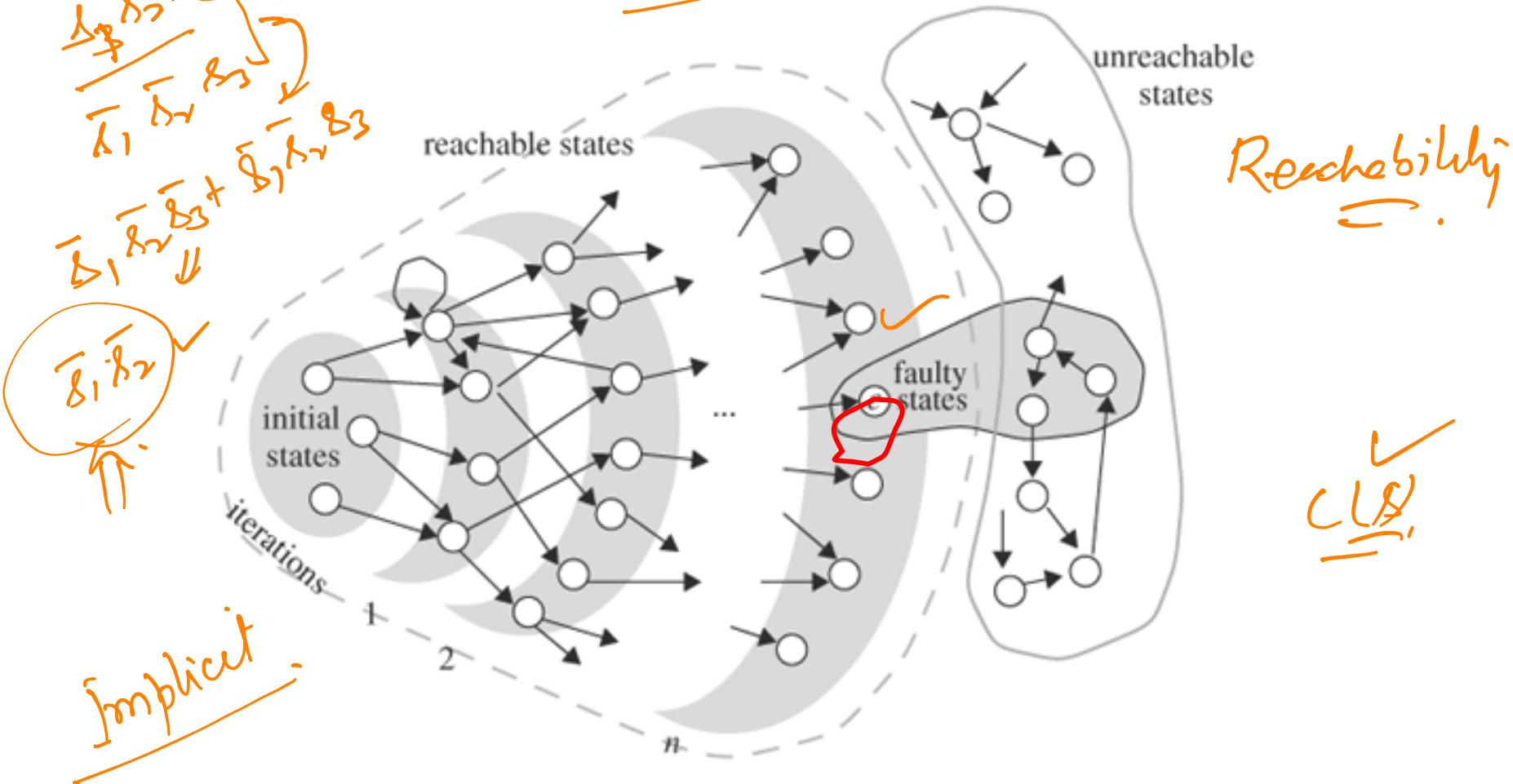

# Thank You

